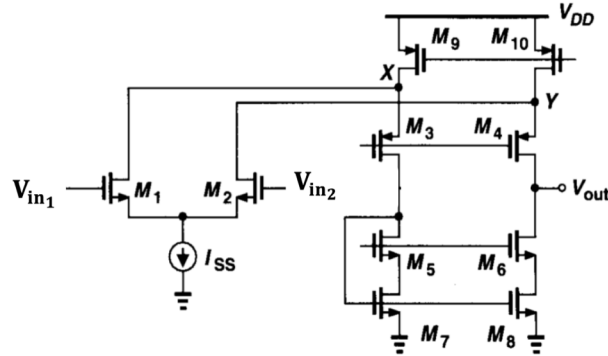


### Problem 3: Folded Cascode Amplifier

In this problem, you may neglect body effect.

Consider the folded cascode differential amplifier below. Assume  $I_9 = I_{10} = I_{SS}$ , and all transistor pairs ( $M_1$  and  $M_2$ ,  $M_3$  and  $M_4$ ,  $M_5$  and  $M_6$ ,  $M_7$  and  $M_8$ ,  $M_9$  and  $M_{10}$ ,  $M_{1p}$  and  $M_{2p}$ ) are matched. Assume  $V_{DD} = 1.8V$ ,  $|V_{th}| = 0.4V$ ,  $V_{ov} = (V^*) = 0.1V$  for all transistors,  $\lambda_p = \lambda_n \neq 0$  and  $g_m r_o \gg 1$ . Express your answers in terms of  $g_m$  and  $r_o$  if needed, where  $g_m = \frac{I_{SS}}{V^*}$  and  $r_o = \frac{1}{\lambda \frac{I_{SS}}{2}}$ . The current source  $I_{SS}$  is an ideal current source but needs a minimum voltage of  $V_{ov} = 0.1V$  to operate.




- a) (3 points) Find the differential gain of this circuit. Express your answer in terms of small signal parameters.

$$A_{v_{diff}} =$$

- c) (2 points) What are the highest and lowest allowed common-mode input level of this amplifier? You can assume you can set the bias voltages of the gates of  $M_{3-6}$  to any allowed desired value.

$$V_{i_{CM_{High}}} = \quad \quad \quad V_{i_{CM_{Low}}} =$$

 - d) (2 points) For the modified amplifier below, what are the highest and lowest allowed common-mode input level? You can assume you can set the bias voltages of the gates of  $M_{3-6}$  to any allowed desired value.



$$V_{iCM_{High}} =$$

$$V_{iCM_{Low}} =$$

## Problem 1 - Stability Compensation [14 pts]

For this problem, all the transistors shown in the figures are in the saturation region with the same  $g_m$  and  $r_o$ . You can assume that  $g_m r_o \gg 1$ , and you can ignore all the other parasitic capacitors that are not specified or shown in the figures.

Below is the diagram of a simple 2-stage amplifier designed for a unity-gain voltage amplifier that drives a load capacitor  $C_L$ .  $V_B$  is a DC voltage.  $C_C$  is the compensation capacitor, and we have  $C_C > C_L$ .

 


Figure 1: Diagram of the 2-Stage Amplifier

- (a) (2 pts) The connection of this unity-gain voltage amplifier is not complete yet. Circle around the correct answer to finalize the connection.

Connect $v_{out}$ to:	$v_{i1}$	$v_{i2}$
-----------------------	----------	----------

- (b) (4 pts) Draw the bode plot of the loop gain  $LG(s)$  of the circuit shown in Figure 2. Clearly label and specify the DC loop gain, the poles and zeros using  $g_m$ ,  $r_o$ ,  $C_C$  and  $C_L$ .

 


Figure 2: Diagram of the 2-Stage Amplifier

(Additional space for Problem 1 part b)

 


Figure 3: Diagram of the 2-Stage Amplifier

- (c) (2 pts) You decided to cancel out the zero in the original loop gain expression, so you placed a resistor as shown in figure 4. What is the resistance  $R_C$  to cancel the zero?

 


Figure 4: Diagram of the 2-Stage Amplifier with Additional Resistor

$$R_C =$$

- (d) (2 pts) You decided to add a source follower to drive  $M_6$  so your design has a class-AB output. The design parameters (transistor sizes,  $I_D, g_m, r_o, R_C, C_C, C_L$ ) don't change compared to the design shown in Figure 4. The  $g_m$  and  $r_o$  of  $M_7$  are both the same as those of other transistors. What is the DC loop gain now?

 


Figure 5: Diagram of the 2-Stage Amplifier with Class-AB Output

$$LG_0 =$$



- (e) (4 pts) Draw the bode plot of your loop gain  $LG(s)$  with class-AB output. Clearly label and specify the DC loop gain, the poles and zeros using  $g_m, r_o, R_C, C_C$  and  $C_L$


 


Figure 6: Diagram of the 2-Stage Amplifier with Class-AB Output
 
### 3 Bandgap References

Consider the bandgap circuit shown below, which uses PNP BJTs available in a CMOS process.



Don't worry about the BJTs,  
just treat them as diodes as was  
done in class.

The emitter area of  $Q_1$  is  $N$  times larger than that of  $Q_2$ , and the dimensions of the PMOS devices are equal. Assume that the amplifier is ideal and the base current of the BJTs is zero.

- (a) (2 points) What is the ratio of the currents through the right and left branches of the circuit  $I_{Q1}/I_{Q2}$ ?

$$\frac{I_{Q1}}{I_{Q2}} =$$

- (b) (2 points) This circuit generates a PTAT current. Find an expression for the current flowing through  $R_1$ .

$$I_{R1} =$$

- (c) (3 points) With a correct choice of  $R_1$  and  $R_2$ , this circuit can also generate a temperature independent bandgap voltage at one of its nodes. Identify and mark this node on the schematic on the previous page. Then write an expression for  $V_{bg}$ .


$$V_{bg} =$$

- (d) (2 points) Now, determine the ratio of  $R_1/R_2$  such that the node identified in part (c) becomes a bandgap reference voltage.

$$\frac{R_1}{R_2} =$$

 
**Problem 5 (13 pts; 15pts)**

Three identical common source stages ( $M_1$ ,  $M_2$  and  $M_3$  are identical) are cascaded as shown below. You may write your answers for all parts in terms of  $gm$ ,  $C_{gs}$ ,  $R_L$ ,  $R_{FB}$ . You should assume that  $R_{FB} \gg R_L$  and  $r_o = \infty$  to simplify your calculations.



- a) (2pts) Compute the DC loop gain of the above circuit.

Loop Gain =

 


- b) (3pts) Assume you compensate with a capacitor  $C_1$ . Write the location of each of the 3 **open-loop** poles. Consider only  $C_1$  and  $C_{GS}$  of each device.

$$p_1 =$$

$$p_2 =$$

$$p_3 =$$

 - c) (4pts) What is the value of  $C_1$  to compensate the loop for 45 degrees phase margin?  
Consider only  $C_1$  and  $C_{GS}$  of each device. *Hint: assume that the phase of a pole looks like the linear approximation below:*



$C_1 =$