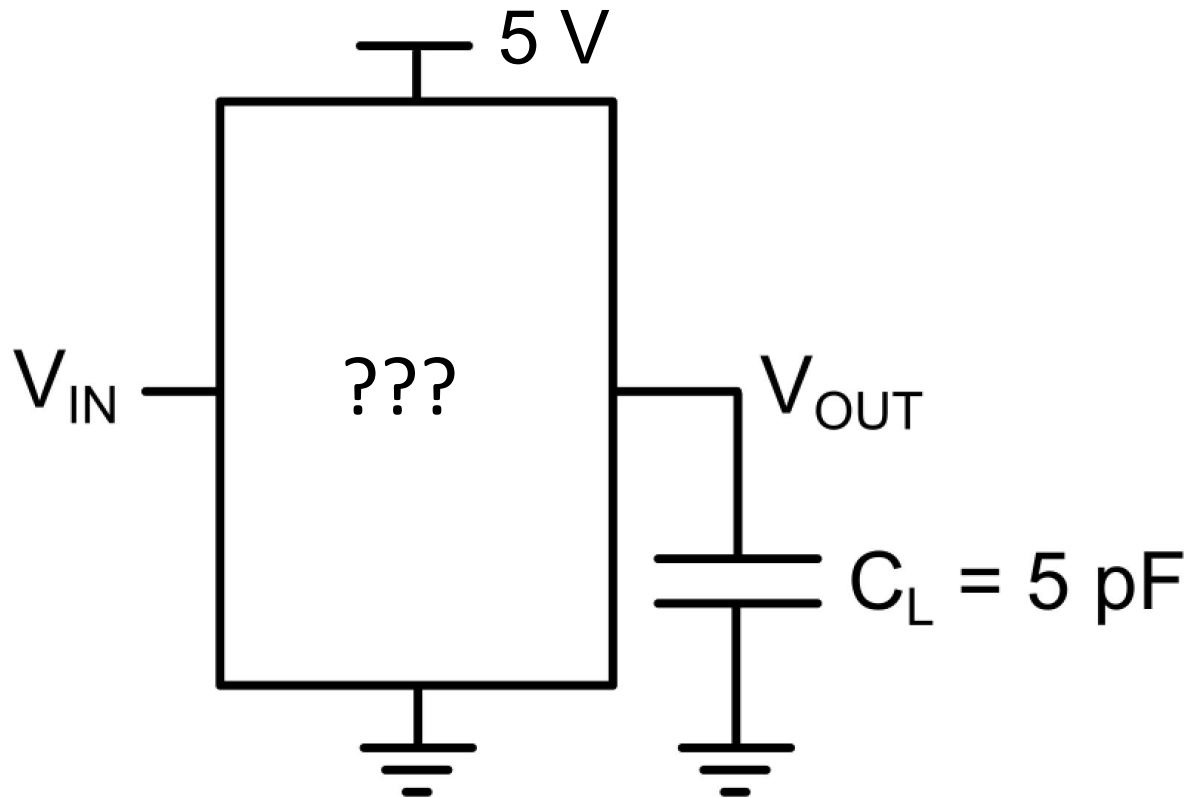


“Design Procedure:” Example


- **Goal:** Design an amplifier to drive a 5 pF load that provides gain > 10 , bandwidth > 1 MHz, with an output swing within 500 mV of +5 V / 0 V supply rails



Step 0: What can this process technology do?

Characterize the small-signal parameters of devices in the technology you are using.

- Short-channel devices (example):

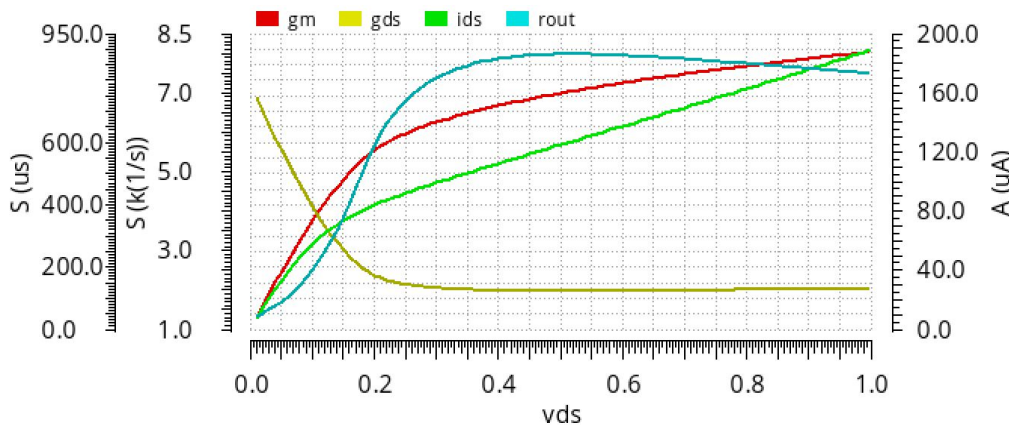


Use simulator to
characterize
small-signal parameters
vs. bias point

Step 0: What can this process technology do?

Characterize the small-signal parameters of devices in the technology you are using.

- Short-channel devices (example):

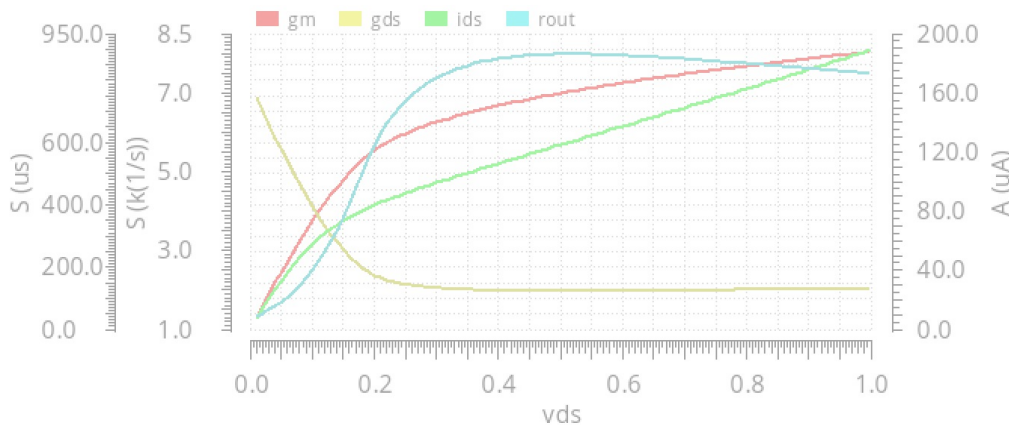

Use simulator to
characterize
small-signal parameters
vs. bias point

- Long-channel devices (square-law model holds):

Hand calculations suffice for most parameters:

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$


$$g_m \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \approx \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$r_o = \frac{1}{\lambda I_D}$$

Step 0: What can this process technology do?

Characterize the small-signal parameters of devices in the technology you are using.

- Short-channel devices (example):

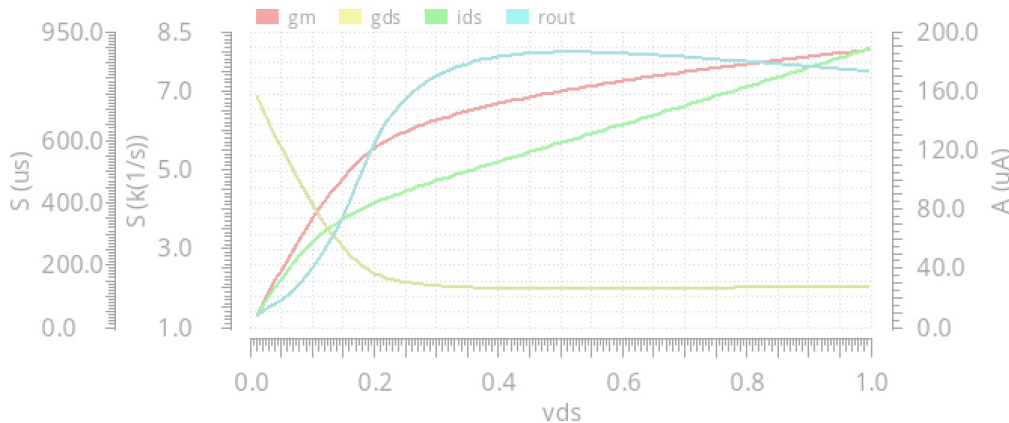

Use simulator to
characterize
small-signal parameters
vs. bias point

- Long-channel devices (square-law model holds):

Hand calculations suffice for most parameters:

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$g_m \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \approx \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$r_o = \frac{1}{\lambda I_D}$$

This process technology:

Parameter	NMOS	PMOS
VTO	0.8 V	-0.8 V
KP	90 $\mu\text{A}/\text{V}^2$	30 $\mu\text{A}/\text{V}^2$
LAMBDA	0.01 V^{-1}	0.02 V^{-1}

Step 0: What can this process technology do?

Characterize the small-signal parameters of devices in the technology you are using.

▪ Full process parameter list

Parameter	NMOS	PMOS	
Model Level	3 (in HSPICE)	3 (in HSPICE)	
VTO	0.8 V	-0.8 V	Threshold voltage
KP	90 $\mu\text{A}/\text{V}^2$	30 $\mu\text{A}/\text{V}^2$	Transconductance
GAMMA	0.8 \sqrt{V}	0.4 \sqrt{V}	Bulk threshold parameter
LAMBDA	0.01 V^{-1}	0.02 V^{-1}	Channel length modulation
TOX	200 Å	200 Å	Gate oxide thickness
XJ	0.5 μm	0.5 μm	Junction depth
LD	0.3 μm	0.3 μm	Lateral diffusion length
PHI	0.7 V	0.6 V	Surface potential
NSUB	$3.33 \times 10^{16} \text{ cm}^{-3}$	$3.33 \times 10^{15} \text{ cm}^{-3}$	Substrate doping density
RSH	0 Ω	0 Ω	Drain/source siddution sheet resistance
CGSO	500 pF/m	500 pF/m	Gate-source overlap capacitance
CGDO	500 pF/m	500 pF/m	Gate-drain overlap capacitance
CGBO	0 F/m	0 F/m	Gate-bulk overlap capacitance
CJ	300 $\mu\text{F}/\text{m}^2$	300 $\mu\text{F}/\text{m}^2$	Bulk junction cap, 0V, bottom
MJ	0.5	0.5	Bulk junction grading coeff., bottom
CJSW	0 F/m	0 F/m	Bulk junction cap, 0V, sidewall
MJSW	0.33	0.33	Bulk junction grading coeff., sidewall


Process / SPICE parameters for NMOS / PMOS transistors.

Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.

- Topology choice sets achievable G_m and R_{out}

From
lecture:

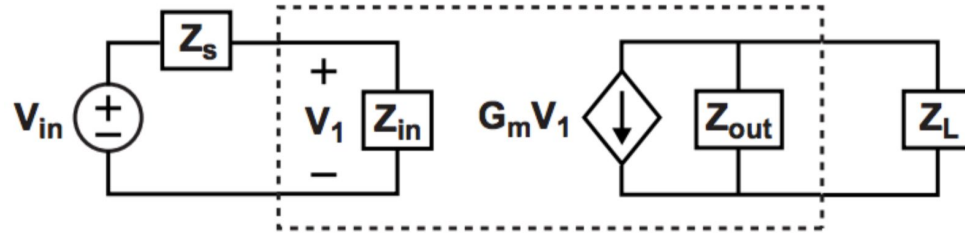


Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.

- Topology choice sets achievable G_m and R_{out}

From
lecture:

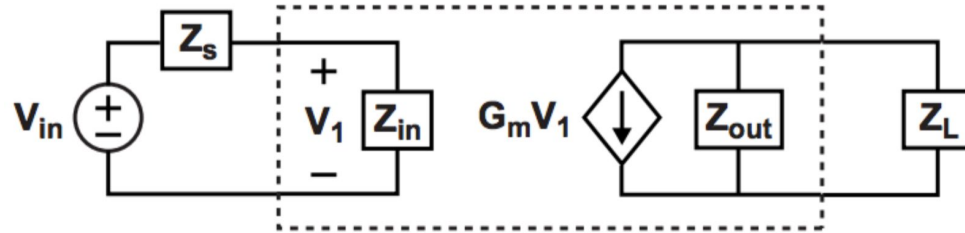


- What do G_m and R_{out} need to be relative to a single device?

Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.

- Topology choice sets achievable G_m and R_{out}

From
lecture:

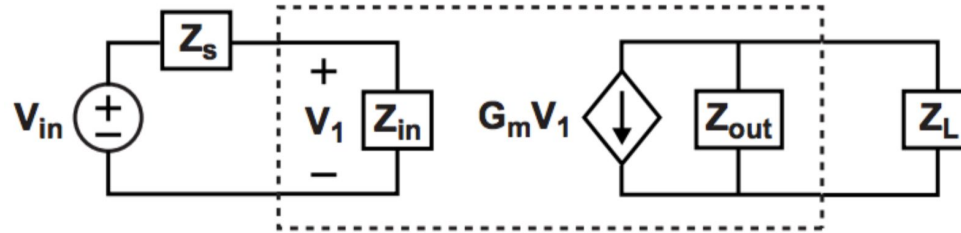

- What do G_m and R_{out} need to be relative to a single device?

Single device performance

Swing constraint: $V_{DS} > V_{GS} - V_T$

	$V_{GS}=1V, W/L=5$		$V_{GS}=1.3V, W/L=20$	
	NMOS	PMOS	NMOS	PMOS
	9 μA	3 μA	0.2 mA	75 μA
	90 μS	30 μS	0.9 mS	0.3 mS
	11 M Ω	17 M Ω	0.4 M Ω	0.7 M Ω


g_m in the 100s of μS , r_o in the 100s of k Ω

Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.

- Topology choice sets achievable G_m and R_{out}

From
lecture:

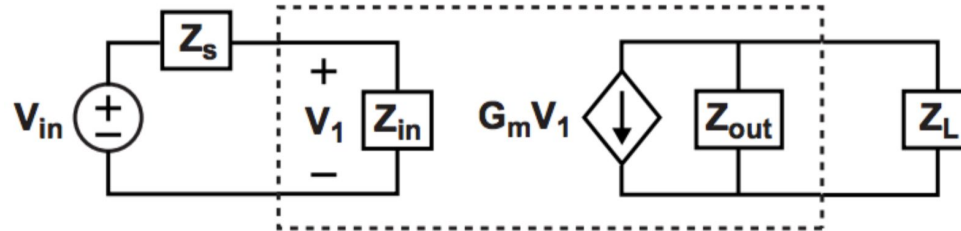

- What do G_m and R_{out} need to be relative to a single device?

Single device performance

Swing constraint: $V_{DS} > V_{GS} - V_T$

	$V_{GS}=1V, W/L=5$		$V_{GS}=1.3V, W/L=20$	
	NMOS	PMOS	NMOS	PMOS
	9 μA	3 μA	0.2 mA	75 μA
	90 μS	30 μS	0.9 mS	0.3 mS
	11 M Ω	17 M Ω	0.4 M Ω	0.7 M Ω

Requirements

Bandwidth constraint:

$$f_{BW} \approx \frac{1}{2\pi R_{out} C_L} \geq 1 \text{ MHz}$$

$$R_{out} \leq \frac{1}{2\pi \cdot 1 \text{ MHz} \cdot 5 \text{ pF}} = 32 \text{ k}\Omega$$

Gain constraint:

$$A_V = G_m R_{out} \geq 10 \rightarrow G_m \geq \frac{10}{R_{out}} = 0.31 \text{ mS}$$


g_m in the 100s of μS , r_o in the 100s of $k\Omega$

Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.

- Topology choice sets achievable G_m and R_{out}

From lecture:

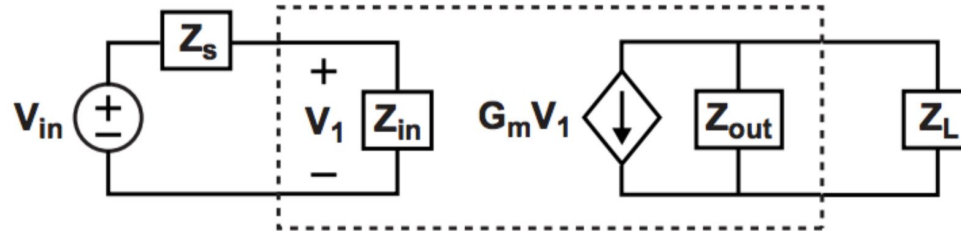

- What do G_m and R_{out} need to be relative to a single device?

Single device performance

Swing constraint: $V_{DS} > V_{GS} - V_T$

	$V_{GS}=1V, W/L=5$		$V_{GS}=1.3V, W/L=20$	
	NMOS	PMOS	NMOS	PMOS
	9 μA	3 μA	0.2 mA	75 μA
	90 μS	30 μS	0.9 mS	0.3 mS
	11 M Ω	17 M Ω	0.4 M Ω	0.7 M Ω

g_m in the 100s of μS , r_o in the 100s of k Ω

Requirements

Bandwidth constraint:

$$f_{BW} \approx \frac{1}{2\pi R_{out} C_L} \geq 1 \text{ MHz}$$

$$R_{out} \leq \frac{1}{2\pi \cdot 1 \text{ MHz} \cdot 5 \text{ pF}} = 32 \text{ k}\Omega$$

Gain constraint:


$$A_V = G_m R_{out} \geq 10 \rightarrow G_m \geq \frac{10}{R_{out}} = 0.31 \text{ mS}$$

g_m about right, r_o needs to be smaller


Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.


Common Source
Amplifier

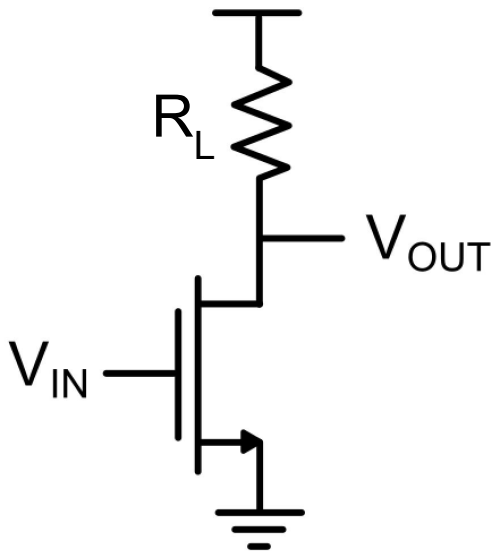

Common Source Amplifier w/
Degeneration

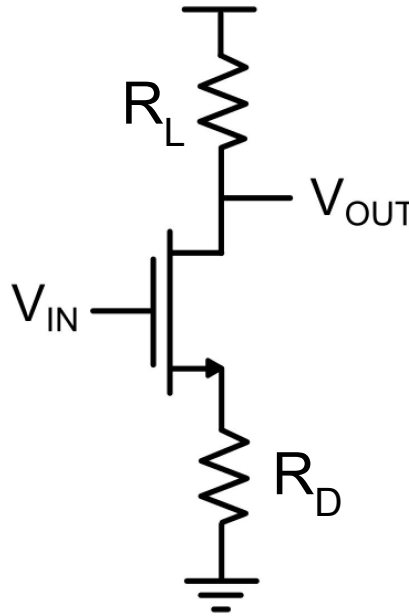


Source Follower

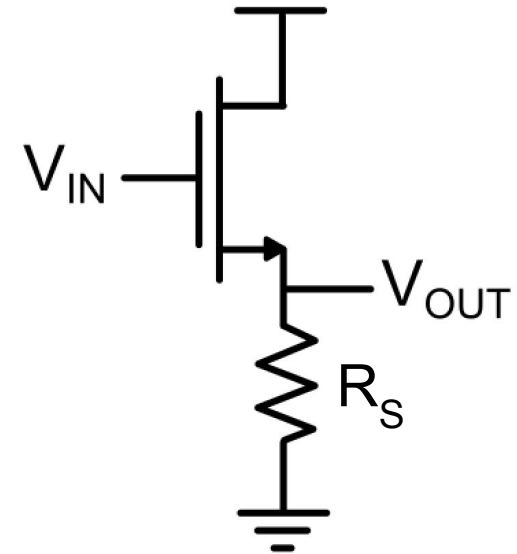


Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.


Common Source
Amplifier

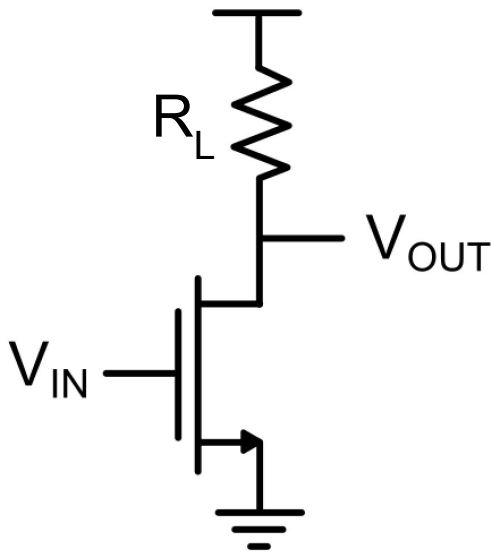

Common Source Amplifier w/
Degeneration

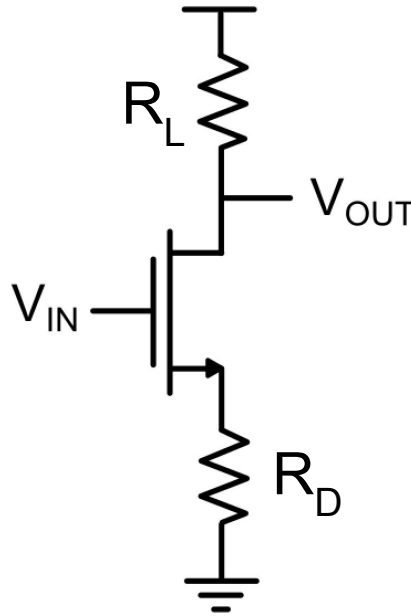

Source Follower

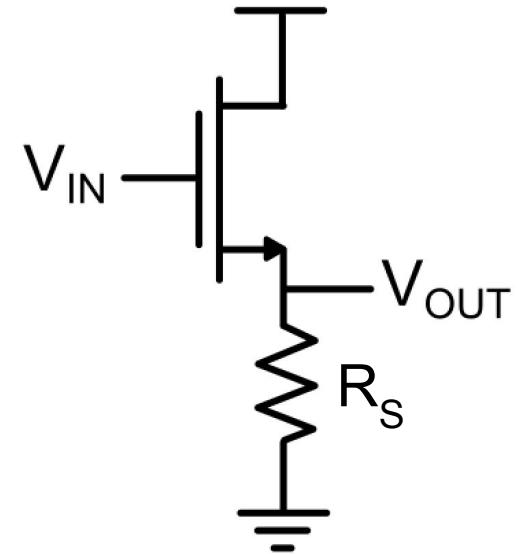


	Equation	Effect
G_m	g_m	Same
R_{out}	$r_o \parallel R_L$	↓


Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.


Common Source
Amplifier

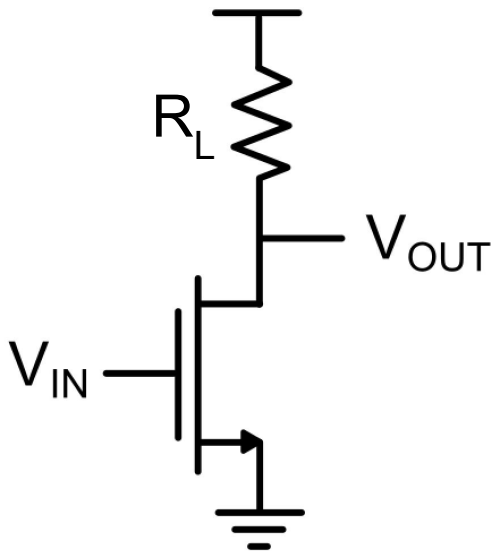

Common Source Amplifier w/
Degeneration

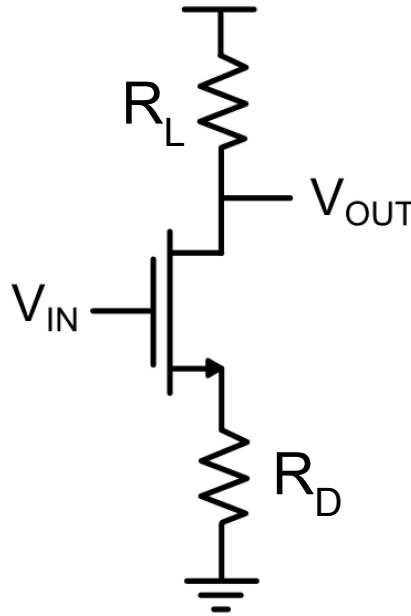

Source Follower

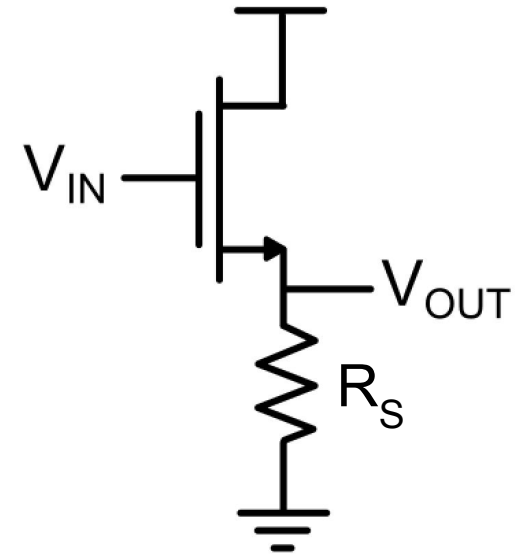


	Equation	Effect	Equation	Effect
G_m	g_m	Same	$g_m / (1 + g_m R_D)$	↓
R_{out}	$r_o \parallel R_L$	↓	$(r_o (1 + g_m R_D)) \parallel R_L$	Varies


Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.


Common Source Amplifier

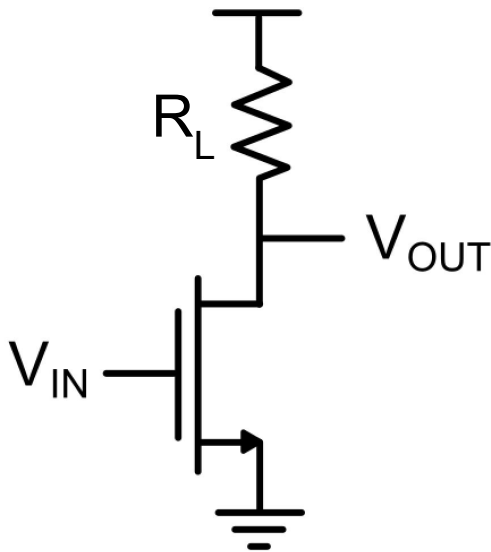

Common Source Amplifier w/ Degeneration

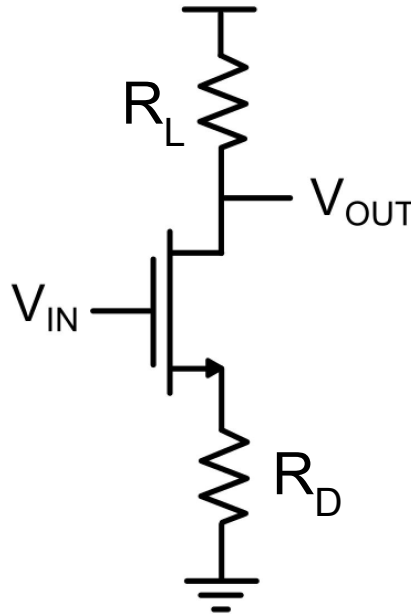

Source Follower

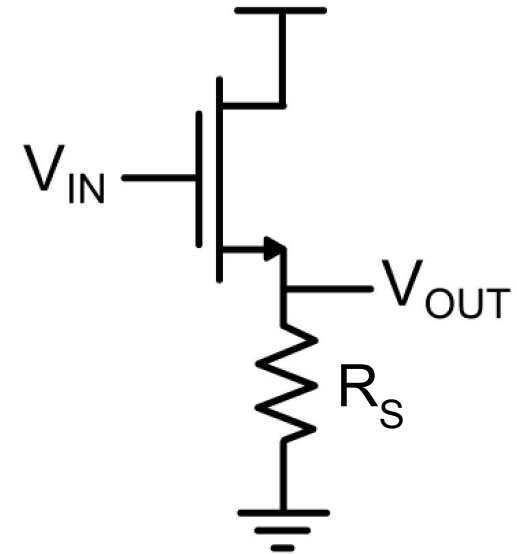


	Equation	Effect	Equation	Effect	Equation	Effect
G_m	g_m	Same	$g_m / (1 + g_m R_D)$	↓	g_m	Same
R_{out}	$r_o \parallel R_L$	↓	$(r_o (1 + g_m R_D)) \parallel R_L$	Varies	$R_S \parallel (1/g_m)$	↓ ↓


Step 1: What topology should you use?

Find out how target specs impact specific parameters, and choose topology accordingly.


Common Source Amplifier

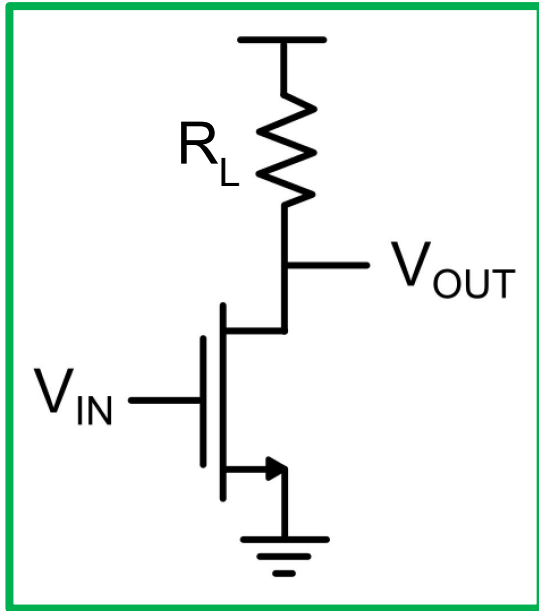

Common Source Amplifier w/ Degeneration

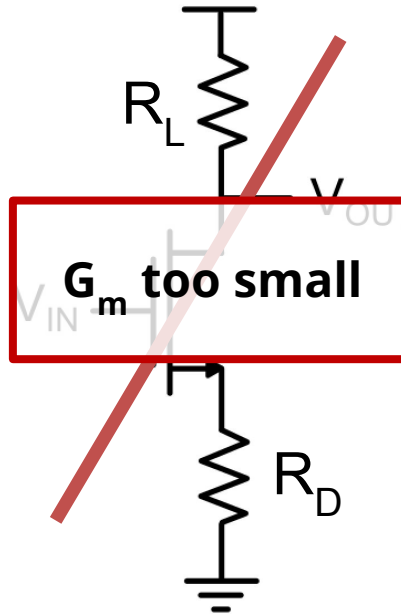

Source Follower

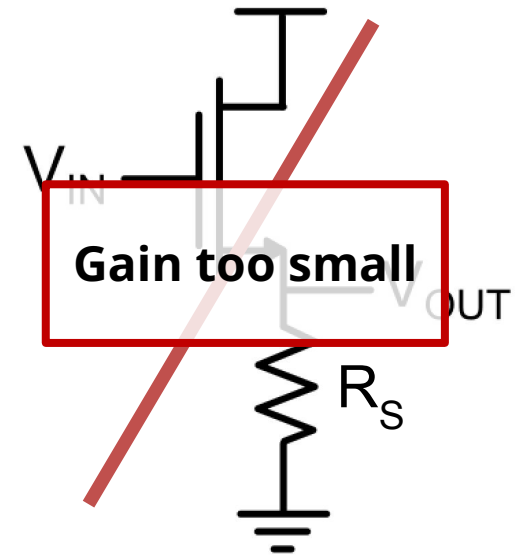


	Equation	Effect	Equation	Effect	Equation	Effect
G_m	g_m	Same	$g_m / (1 + g_m R_D)$	↓	g_m	Same
R_{out}	$r_o \parallel R_L$	↓	$(r_o (1 + g_m R_D)) \parallel R_L$	Varies	$R_S \parallel (1/g_m)$	↓ ↓

Step 2: What parameters and constraints exist?

Make a list of relevant equations and sort out how many “free” variables you really have.

Common Source
Amplifier

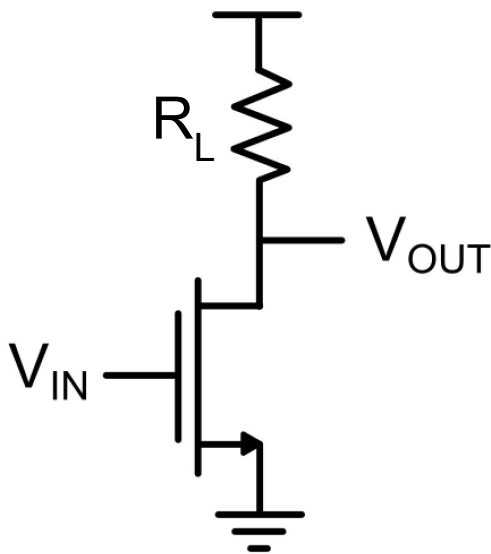


Design constraints	Relevant equations
Gain > 10	$A_V = G_m R_{out} = g_m (r_o R_L)$
BW > 1 MHz	$f_{BW} \approx 1/(2\pi(r_o R_L)C_L)$
Output swing within 500 mV of supply rails	$V_{OUT} > V_{GS} - V_T$ $V_{min} = V_{GS} - V_T$

Step 2: What parameters and constraints exist?

Make a list of relevant equations and sort out how many “free” variables you really have.

Common Source
Amplifier

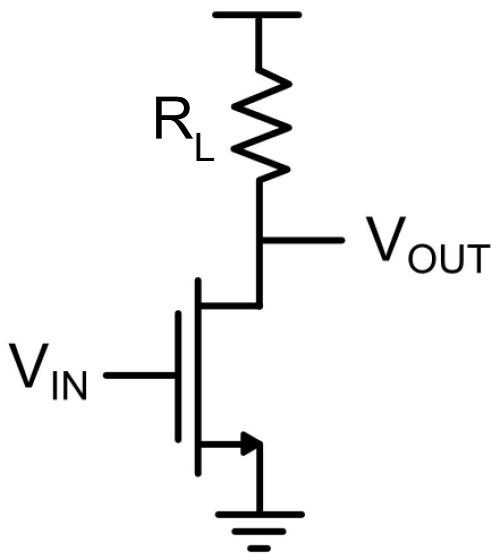


Design constraints	Relevant equations
Gain > 10	$A_V = G_m R_{out} = g_m (r_o R_L)$
BW > 1 MHz	$f_{BW} \approx 1/(2\pi(r_o R_L)C_L)$
Output swing within 500 mV of supply rails	$V_{OUT} > V_{GS} - V_T$ $V_{min} = V_{GS} - V_T$

“Free” variables: V_{GS} , W/L , V_{OUT} , I_{DS} , R_L , ???

Step 2: What parameters and constraints exist?

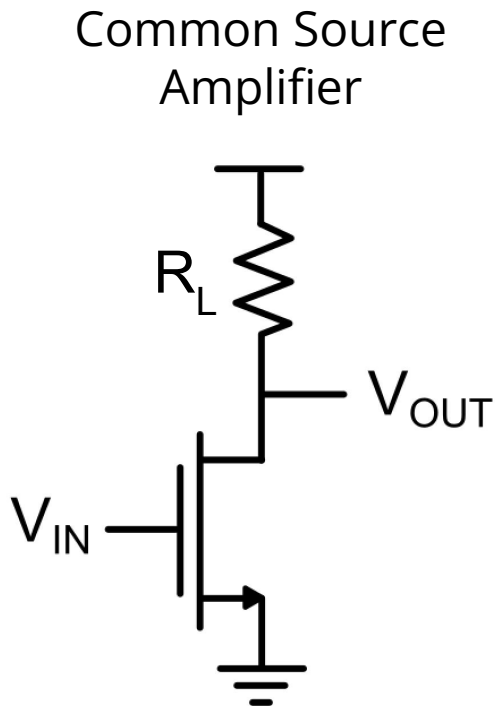Make a list of relevant equations and sort out how many “free” variables you really have.



Design constraints	Relevant equations
Gain > 10	$A_V = G_m R_{out} = g_m (r_o R_L)$
BW > 1 MHz	$f_{BW} \approx 1/(2\pi(r_o R_L)C_L)$
Output swing within 500 mV of supply rails	$V_{OUT} > V_{GS} - V_T$ $V_{min} = V_{GS} - V_T$

“Free” variables: V_{GS} , W/L , V_{OUT} , I_{DS} , R_L , ???

$$R_L = \frac{V_{DD} - V_{OUT}}{I_{DS}}$$

Full equations for R_{out} and G_m :


$$R_{out} = r_o || R_L = \frac{1}{I_{DS}} \frac{V_{DD} - V_{OUT}}{(1 + \lambda(V_{DD} - V_{OUT}))} \approx \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

Step 2: What parameters and constraints exist?

Make a list of relevant equations and sort out how many “free” variables you really have.

Common Source Amplifier

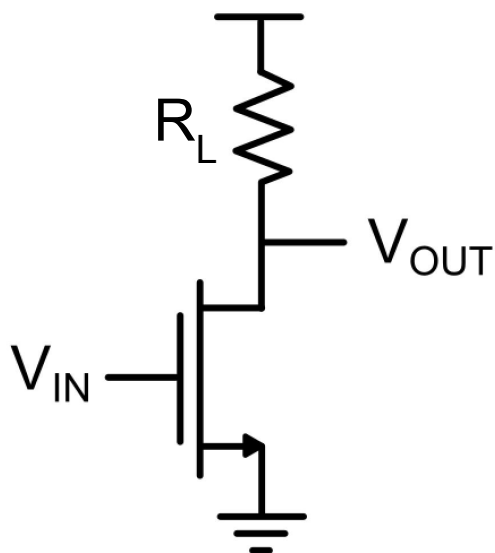

Design constraints	Relevant equations
Gain > 10	$A_V = G_m R_{out} = g_m (r_o R_L)$
BW > 1 MHz	$f_{BW} \approx 1/(2\pi(r_o R_L)C_L)$
Output swing within 500 mV of supply rails	$V_{OUT} > V_{GS} - V_T$ $V_{min} = V_{GS} - V_T$

Free variables: V_{GS} , W/L , V_{OUT} , I_{DS} , R_L

$$R_L = \frac{V_{DD} - V_{OUT}}{I_{DS}}$$

Full equations for R_{out} and G_m :

$$R_{out} = r_o || R_L = \frac{1}{I_{DS}} \frac{V_{DD} - V_{OUT}}{(1 + \lambda(V_{DD} - V_{OUT}))} \approx \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \quad \longrightarrow \quad V_{GS} - V_T \leq 500 \text{ mV}$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \quad \longrightarrow \quad V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

$$\text{Gain: } G_m R_{out} \geq 10$$

$$\text{Bandwidth: } R_{out} \leq 32 \text{ k}\Omega$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \quad \longrightarrow \quad V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

Gain: $G_m R_{out} \geq 10$

Bandwidth: $R_{out} \leq 32 \text{ k}\Omega$

$$G_m R_{out} = k' \frac{W}{L} (V_{GS} - V_{TH}) \frac{2}{k' \frac{W}{L} (V_{GS} - V_{TH})^2} \frac{V_{DD} - V_{OUT}}{(1 + \lambda(V_{DD} - V_{OUT}))}$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \rightarrow V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

Gain: $G_m R_{out} \geq 10$

Bandwidth: $R_{out} \leq 32 \text{ k}\Omega$

$$\begin{aligned}
 G_m R_{out} &= \cancel{k' \frac{W}{L} (V_{GS} - V_{TH})} \frac{2}{\cancel{k' \frac{W}{L} (V_{GS} - V_{TH})^2}} \frac{V_{DD} - V_{OUT}}{(1 + \lambda(V_{DD} - V_{OUT}))} \\
 &= \frac{2}{(V_{GS} - V_{TH})} \frac{V_{DD} - V_{OUT}}{(1 + \lambda(V_{DD} - V_{OUT}))}
 \end{aligned}$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \quad \longrightarrow \quad V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

Gain: $G_m R_{out} \geq 10$

Bandwidth: $R_{out} \leq 32 \text{ k}\Omega$

$$G_m R_{out} = k' \frac{W}{L} (V_{GS} - V_{TH}) \frac{2}{k' \frac{W}{L} (V_{GS} - V_{TH})^2} \frac{V_{DD} - V_{OUT}}{(1 + \lambda(V_{DD} - V_{OUT}))}$$

$$10 \leq \frac{2}{(V_{GS} - V_{TH})} \frac{V_{DD} - V_{OUT}}{(1 + \lambda(V_{DD} - V_{OUT}))}$$

$$V_{GS} - V_{TH} \leq \frac{2}{10} \frac{5V - 2.5V}{(1 + 0.01 \text{ V}^{-1}(5V - 2.5V))} \approx 500 \text{ mV}$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \quad \longrightarrow \quad V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

$$\text{Gain: } G_m R_{out} \geq 10$$

Bandwidth $R_{out} \leq 32 \text{ k}\Omega$

:

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \quad \longrightarrow \quad V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

$$\text{Gain: } G_m R_{out} \geq 10$$

Bandwidth $R_{out} \leq 32 \text{ k}\Omega$

:

$$32 \text{ k}\Omega \geq \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \quad \longrightarrow \quad V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

$$\text{Gain: } G_m R_{out} \geq 10$$

Bandwidth $R_{out} \leq 32 \text{ k}\Omega$

:

$$32 \text{ k}\Omega \geq \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

$$32 \text{ k}\Omega \geq \frac{2(2.5\text{V})}{(90 \mu\text{A/V}^2) \frac{W}{L} (0.5\text{V})^2}$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \quad \longrightarrow \quad V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

$$\text{Gain: } G_m R_{out} \geq 10$$

$$\text{Bandwidth } R_{out} \leq 32 \text{ k}\Omega$$

:

$$32 \text{ k}\Omega \geq \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

$$32 \text{ k}\Omega \geq \frac{2(2.5V)}{(90 \mu\text{A}/V^2) \frac{W}{L} (0.5V)^2}$$

$$\frac{W}{L} \geq \frac{2(2.5V)}{32 \text{ k}\Omega \left(90 \mu \frac{\text{A}}{V^2} \right) (0.5V)^2} = 6.9$$

Step 3: How do constraints impact parameters?

Solve equations to find acceptable design parameter ranges.

$$G_m = g_m = k' \frac{W}{L} (V_{GS} - V_{TH})$$

$$R_{out} = \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

1) Swing constraint: $V_{min} \leq 500 \text{ mV}$

$$V_{min} = V_{GS} - V_T \rightarrow V_{GS} - V_T \leq 500 \text{ mV}$$

2) Bandwidth & gain constraints:

$$\text{Gain: } G_m R_{out} \geq 10$$

$$\text{Bandwidth: } R_{out} \leq 32 \text{ k}\Omega$$

$$32 \text{ k}\Omega \geq \frac{2(V_{DD} - V_{OUT})}{k' \frac{W}{L} (V_{GS} - V_{TH})^2}$$

$$32 \text{ k}\Omega \geq \frac{2(2.5\text{V})}{(90 \mu\text{A/V}^2) \frac{W}{L} (0.5\text{V})^2}$$


$$\frac{W}{L} \geq \frac{2(2.5\text{V})}{32 \text{ k}\Omega \left(90 \mu \frac{\text{A}}{\text{V}^2} \right) (0.5\text{V})^2} = 6.9$$

Parameter	Value
W/L	7
V_{GS}	$0.5 \text{ V} + V_{TH} = 1.3 \text{ V}$
I_{DS}	$78 \mu\text{A}$
R_L	$(V_{DD} - V_{OUT}) / I_{DS} = 32 \text{ k}\Omega$

Step 4: Does this actually work?


Verify your design performance in a circuit simulator.

Simulation

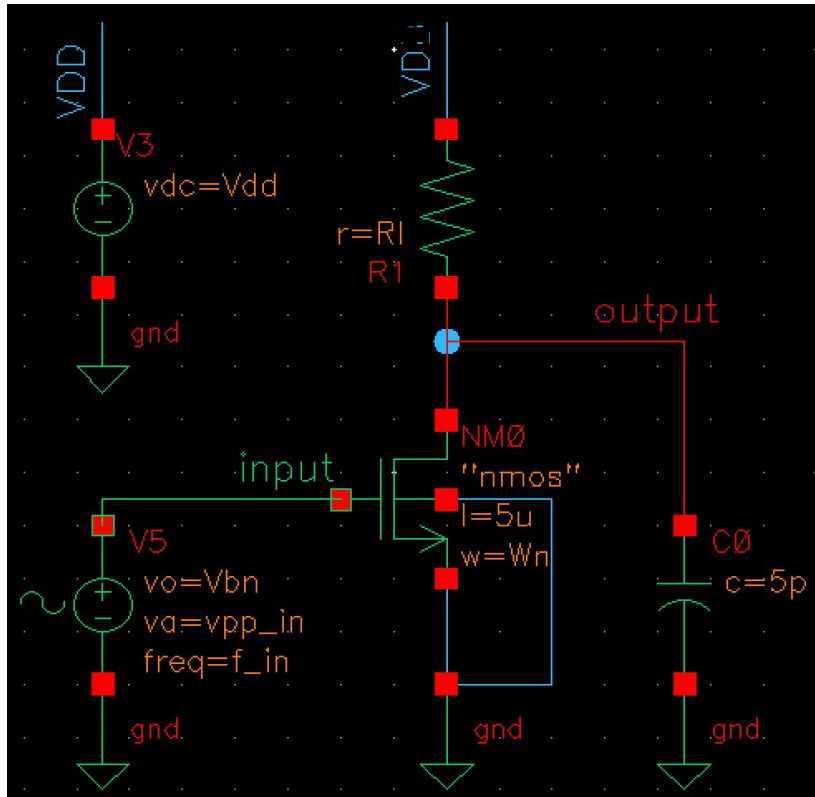


Pretty close! Gain is a little short, so let's increase W/L to boost g_m since R_L dominates R_{OUT} .

AC Response:

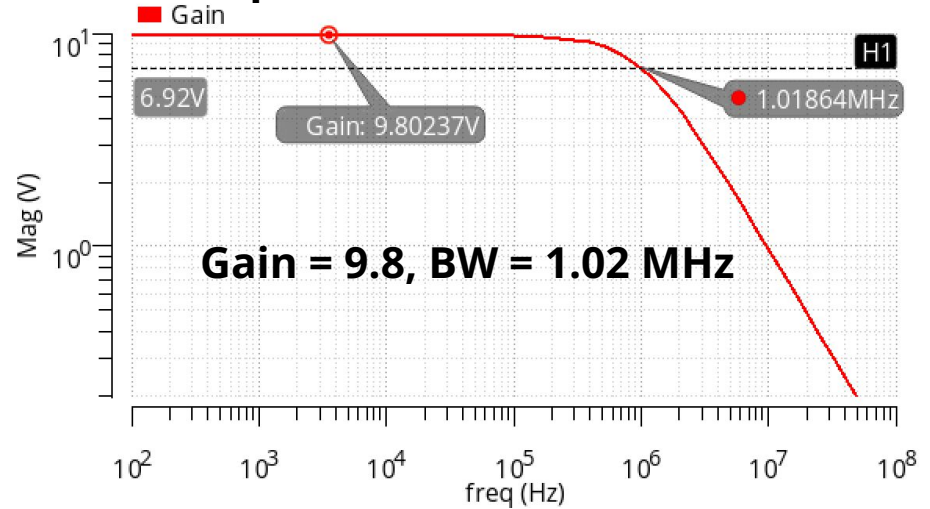


Transient Response:

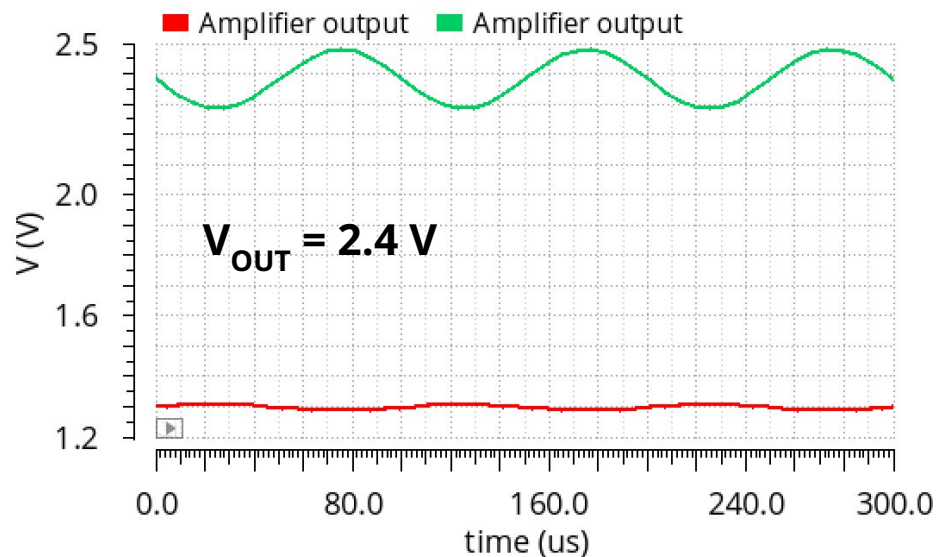


Step 4: Does this actually work?

Verify your design performance in a circuit simulator.


Simulation

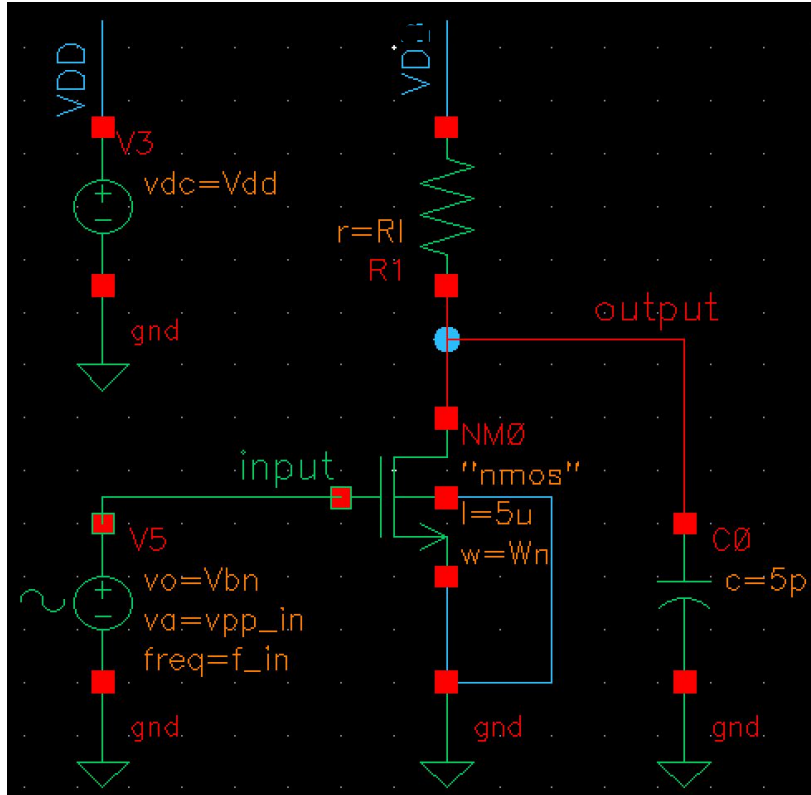

AC Response:

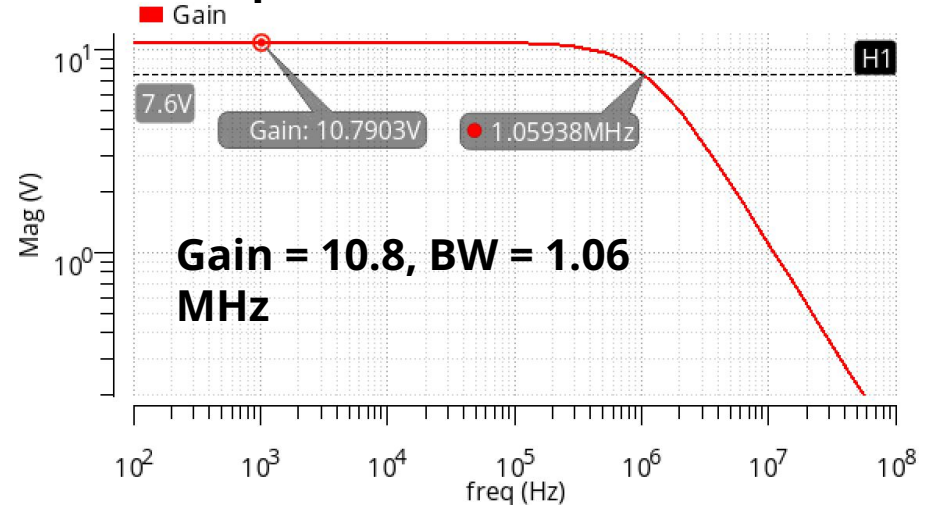

Transient Response:

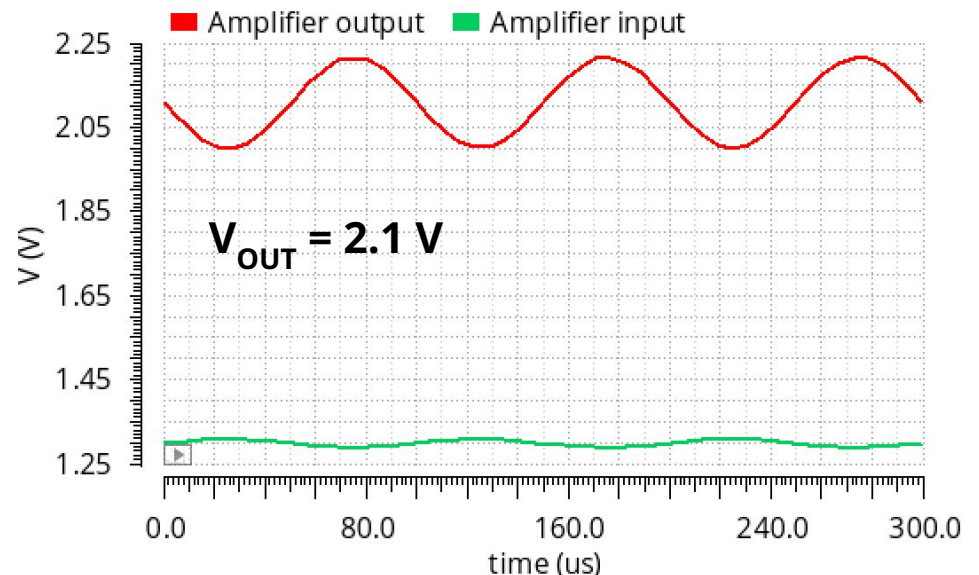

Looks like this will do the job!

Final Note

- Design goals usually involve some sort of optimization:
 - Smallest area
 - Lowest power
 - Highest bandwidth
 - Highest gain
 - Lowest noise
 - “Best” figure of merit (combination of parameters)
- Mathematical solution:
 - Find where derivative of performance metric with respect to design parameters is 0
- Practically:
 - Choose topology carefully for target specifications
 - Identify *key* design parameters