

# EE140 Lab Report: Lab1

Yu Li  
SID: 3039817966

April 2, 2024

## Exercise 1

### • Design and Script

I set up known parameters like gmID, L, etc. Then I use the lookup function for fT, Av and gds. With fu and CL, gm can be calculated, then get ID with gm and gmID. Next I can get JD with lookup method, and finally W.


Script is as follows:

```
1 # EX1
2 # assumptions:
3 gm_ID = 15 # S/A
4 L = 0.1 # 100nm=0.1um
5 CL = 1e-12 # 1 pF
6 fu = 1e9 # 1 GHz
7 VDS = 0.55 # V
8 VSB = 0 # V,
9
10 fT = look_up_vs_gm_id(nch, 'GM_CGG', gm_ID, vds=VDS, l=L) / (2 *
11     np.pi)
11 Av = look_up_vs_gm_id (nch , 'GM_GDS', gm_ID, vds=VDS, l=L)
12 gds = look_up_vs_gm_id(nch, 'GDS', gm_ID, vds=VDS, l=L)
13
14 print(f"gds:{gds}")
15
16 gm = 2 * np.pi * fu * CL
17 print(f"gm:{gm}")
18
19 ro = 1 / gds
20 intrinsic_gain = gm * ro
21
22 print(f"gain :{Av}dB")
23
24 ID = gm / gm_ID
25
26 JD = look_up_vs_gm_id(nch, 'ID_W', gm_ID, vds=VDS, l=L)
27 # print(JD)
28 W = ID / JD
29 print(f"ID:{ID}")
30 VGS = look_up_vgs_vs_gm_id(nch, gm_ID, l=L, vds=VDS)
31
32 print(f"Intrinsic Gain: {intrinsic_gain}")
33 print(f"fT: {fT} Hz")
34 print(f"Width (W): {W} nm")
```

```
35 print(f"Required VGS: {VGS} V")
```

- Cadence simulation

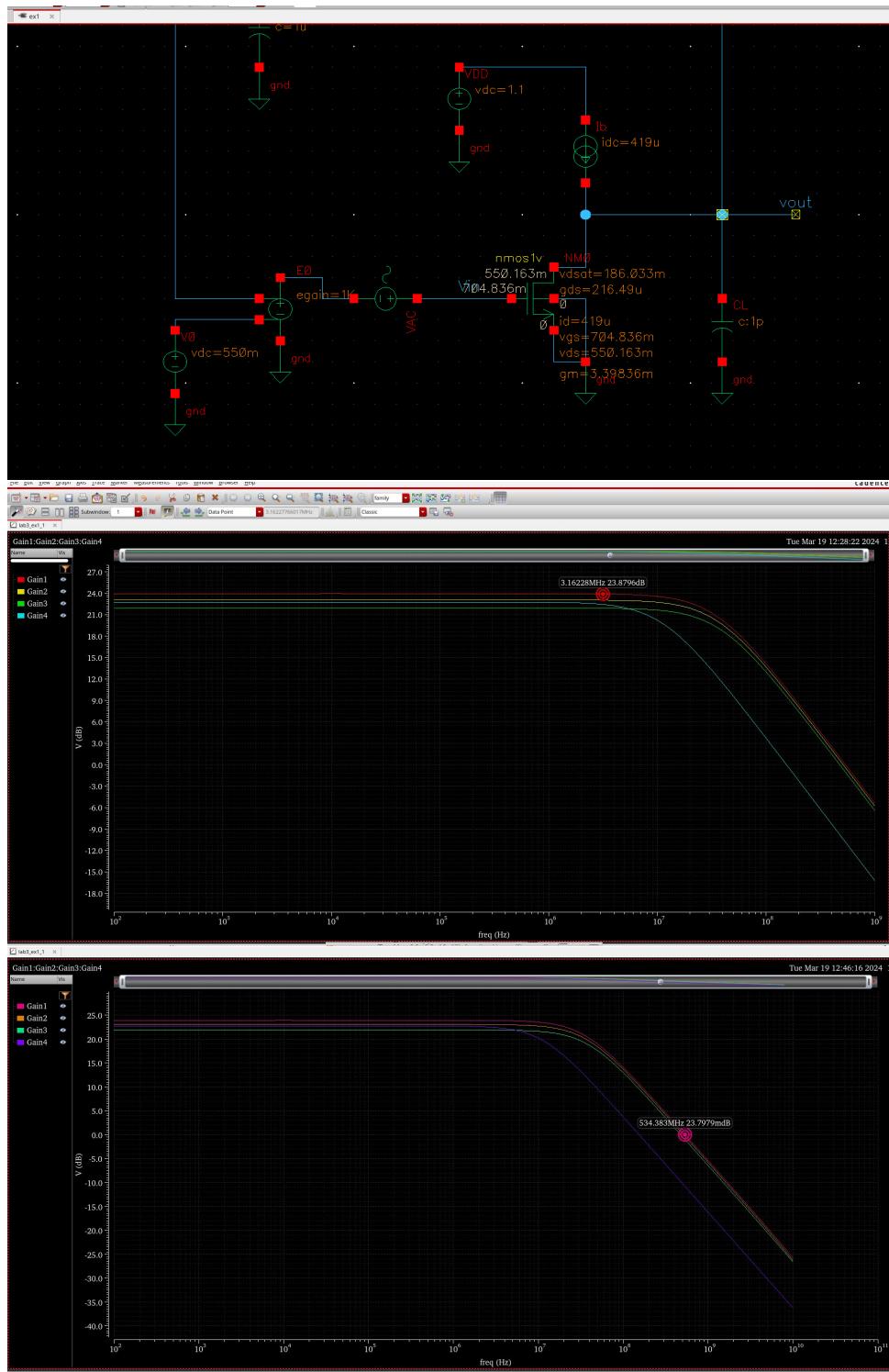
The cadence simulation schematic and bode plot are as follow:  
Gain1 curve is for exercise1.



- Analysis of the results

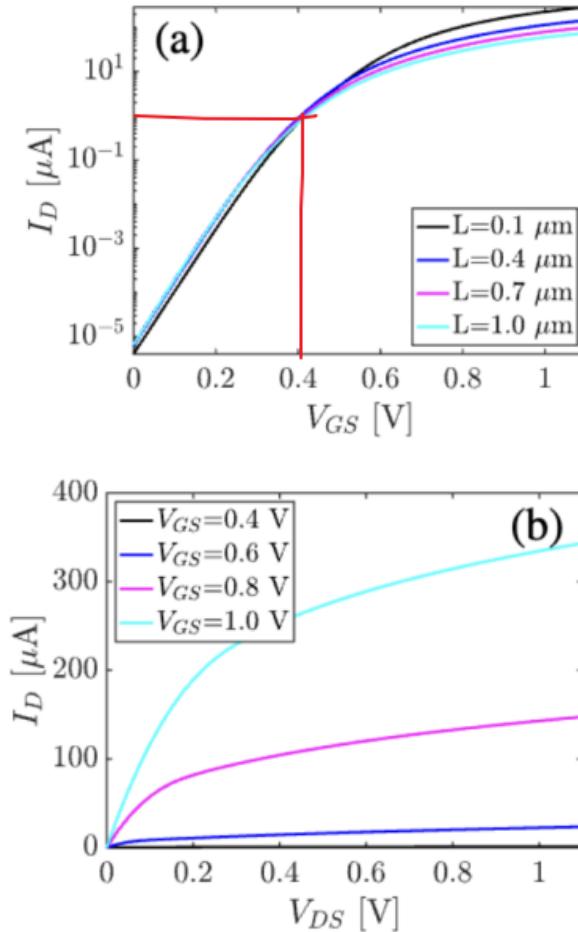
### 1. Question1

The threshold voltage is the VGS when the drain current exceeds 1  $\mu\text{A}$  for a 1  $\mu\text{m}$  width device. So from the figure we can estimate threshold voltage is approximately 0.4V.


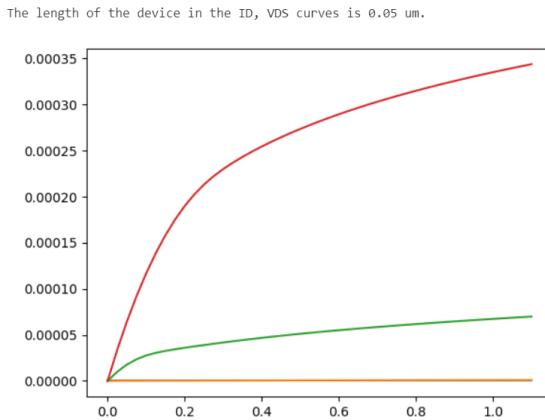
### 2. Question2

According to the code search, the corresponding length of L found is 0.05um.



### 3. Results Analysis

The curves and results displayed by the simulation and the calculated results are listed in the

table below.


Performance	Design result	Simulation result
Gain(dB)	22.37	23.38
Unity gain bandwidth(Hz)	1G (fu)	534.4M
$gm_{ID}(S/A)$	15	8.11
$VGS(V)$	0.54	0.55

It can be found that all the values are relatively close, and the biggest difference is Unity gain bandwidth.
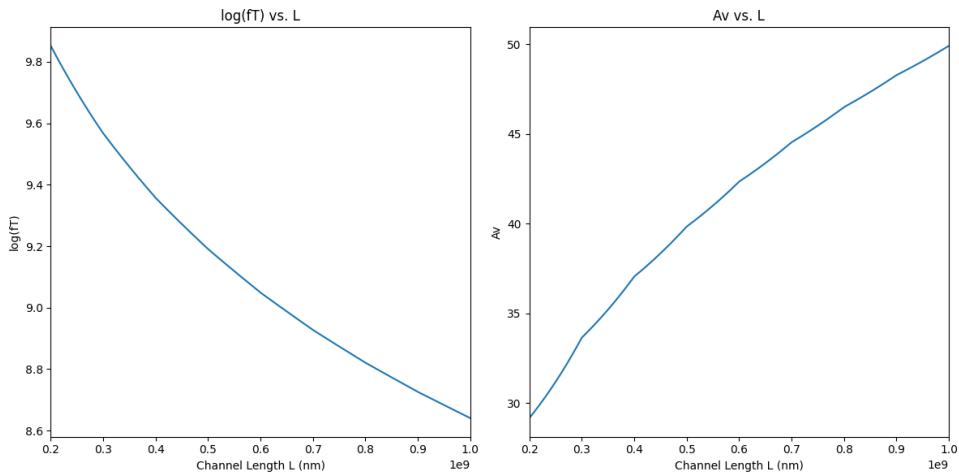
## Exercise 2

- Design and Script

For the design of exercise 2, we must first draw the images of  $f_T$  vs. L and  $A_v$  vs. L according to the question requirements, as shown in the figure below.



In order to satisfy the condition of  $fu=f_T/10$ , we need to select appropriate segments based on the image, and then select the points that meet the conditions in these segments to be the parameters corresponding to the solution we need.

Then we selected the two solutions and repeated the same operations as exercise1 in the script to obtain two sets of results. The next step is to use the same circuit diagram and change the parameters to obtain different Cadence simulation results.

```

1 #EX2
2 gm_ID = 15    # S/A
3 CL = 1e-12   # 1 pF
4 fu = 5e8     # 500 MHz
5 VDS = 0.55   # V
6 VSB = 0      # V
7 L_values = np.linspace(0.2, 1.0, 1000)  # Adjusted to a valid
8               number of points
9
10 # Containers for results
11 fT_values = []
12 Av_values = []
13 W_values = []

```

```

13
14 for L in L_values:
15     # Correct function calls
16     fT = look_up_vs_gm_id(nch, 'GM_CGG', gm_ID, vds=VDS, l=L) / (2
17         * np.pi)
18     Av = look_up_vs_gm_id(nch, 'GM_GDS', gm_ID, vds=VDS, l=L) # 
19         Corrected to L
20     gds = look_up_vs_gm_id(nch, 'GDS', gm_ID, vds=VDS, l=L)
21     gm = 2 * np.pi * fu * CL
22     ID = gm / gm_ID
23     JD = look_up_vs_gm_id(nch, 'ID_W', gm_ID, vds=VDS, l=L)
24     W = ID / JD
25     VGS = look_up_vgs_vs_gm_id(nch, gm_ID, l=L, vds=VDS)
26
27     fT_values.append(fT)
28     Av_values.append(Av)
29     W_values.append(W)
30
31 # Find the maximum value of L that satisfies fu      fT/10
32 fT_values = np.array(fT_values)
33 L_max_index = np.where(fT_values >= 10 * fu)[0][-1]
34 L_max = L_values[L_max_index]
35
36 print(f"Maximum value of L that satisfies fu      fT/10:
37 {L_max:.3f}")
38
39 # Plot log(fT) vs. L
40 plt.figure(figsize=(12, 6))
41 L_values_nm = L_values * 1e9
42 plt.subplot(1, 2, 1)
43 plt.plot(L_values_nm, np.log10(fT_values))
44 plt.xlabel('Channel Length L (nm)')
45 plt.ylabel('log(fT)')
46 plt.title('log(fT) vs. L')
47 plt.xlim(L_values_nm.min(), L_values_nm.max())
48
49 # Plot Av vs. L
50 plt.subplot(1, 2, 2)
51 plt.plot(L_values_nm, Av_values)
52 plt.xlabel('Channel Length L (nm)')
53 plt.ylabel('Av')
54 plt.title('Av vs. L')
55 plt.xlim(L_values_nm.min(), L_values_nm.max())
56
57 plt.tight_layout()
58 plt.show()

```

Then we can select two solutions and use script to obtain corresponding parameters.

```

1 gm_ID = 5 # V^(-1)
2 CL = 1e-12 # 1 pF
3 fu = 5e8 # 500 MHz
4 VDS = 0.55 # V
5 VSB = 0 # V
6
7 # Solution 1

```

```

8 L_1 = 0.200 # Maximum value of L that satisfies fu      fT/10
9
10 fT_1 = look_up_vs_gm_id(nch, 'GM_CGG', gm_ID, vds=VDS, l=L_1) / (2
11   * np.pi)
12 Av_1 = look_up_vs_gm_id(nch, 'GM_GDS', gm_ID, vds=VDS, l=L_1)
13 gds_1 = look_up_vs_gm_id(nch, 'GDS', gm_ID, vds=VDS, l=L_1)
14
15 print(f"Solution 1:")
16 print(f"gds: {gds_1}")
17
18 gm_1 = 2 * np.pi * fu * CL
19 print(f"gm: {gm_1}")
20
21 ro_1 = 1 / gds_1
22 intrinsic_gain_1 = gm_1 * ro_1
23 print(f"Av_1:{Av_1}")
24
25 ID_1 = gm_1 / gm_ID
26
27 JD_1 = look_up_vs_gm_id(nch, 'ID_W', gm_ID, vds=VDS, l=L_1)
28 W_1 = ID_1 / JD_1
29 print(f"ID: {ID_1}")
30 VGS_1 = look_up_vgs_vs_gm_id(nch, gm_ID, l=L_1, vds=VDS)
31
32 print(f"Intrinsic Gain: {intrinsic_gain_1}")
33 print(f"fT: {fT_1} Hz")
34 print(f"Width (W): {W_1}um")
35 print(f"Required VGS: {VGS_1} V")
36
37 # Solution 2
38 L_2 = 0.150 # Different L value
39
40 fT_2 = look_up_vs_gm_id(nch, 'GM_CGG', gm_ID, vds=VDS, l=L_2) / (2
41   * np.pi)
42 Av_2 = look_up_vs_gm_id(nch, 'GM_GDS', gm_ID, vds=VDS, l=L_2)
43 gds_2 = look_up_vs_gm_id(nch, 'GDS', gm_ID, vds=VDS, l=L_2)
44
45 print(f"\nSolution 2:")
46 print(f"gds: {gds_2}")
47
48 gm_2 = 2 * np.pi * fu * CL
49 print(f"gm: {gm_2}")
50
51 ro_2 = 1 / gds_2
52 intrinsic_gain_2 = gm_2 * ro_2
53 print(f"Av_2:{Av_2}")
54
55 ID_2 = gm_2 / gm_ID
56
57 JD_2 = look_up_vs_gm_id(nch, 'ID_W', gm_ID, vds=VDS, l=L_2)
58 W_2 = ID_2 / JD_2
59 print(f"ID: {ID_2}")
60 VGS_2 = look_up_vgs_vs_gm_id(nch, gm_ID, l=L_2, vds=VDS)
61
62 print(f"Intrinsic Gain: {intrinsic_gain_2}")
63 print(f"fT: {fT_2} Hz")

```



```

62 print(f"Width (W): {W_2} um")
63 print(f"Required VGS: {VGS_2} V")

```

- Cadence simulation

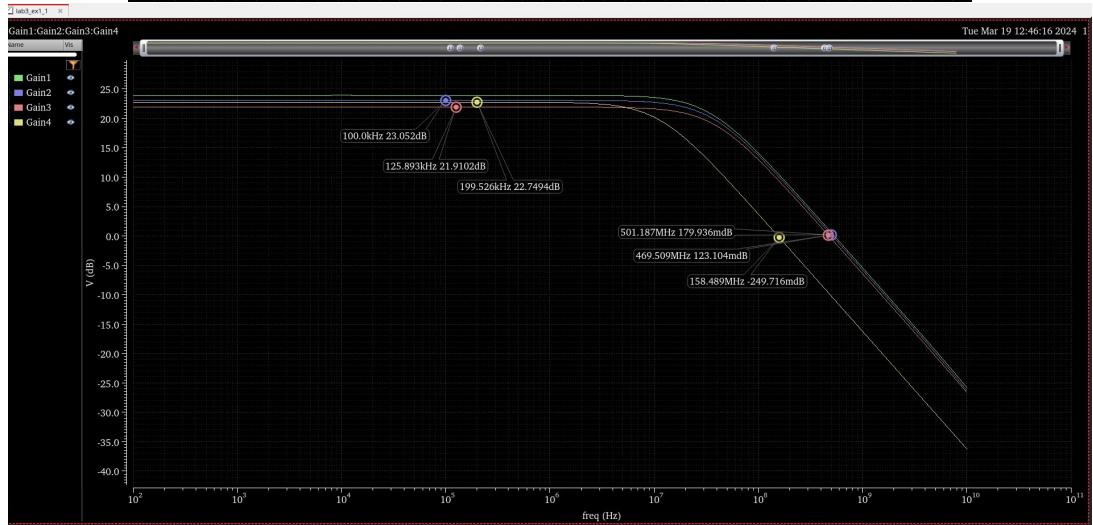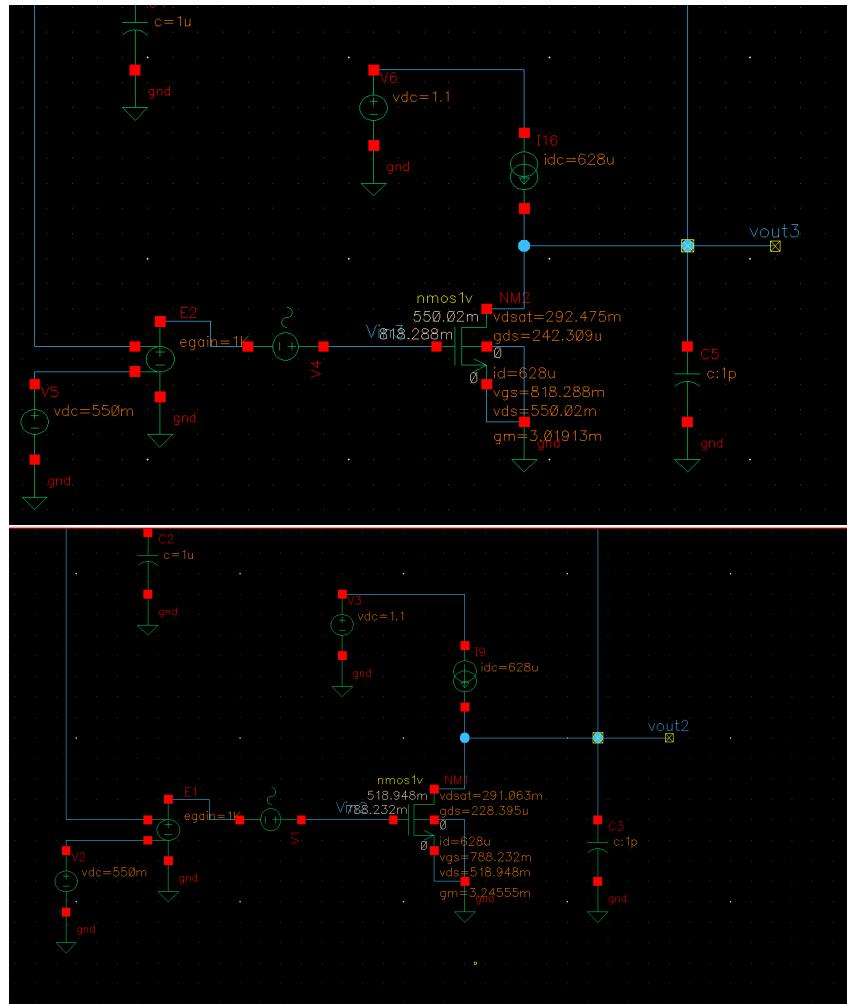Gain2 and Gain3 curves are for exercise2.



- Analysis of the results

The corresponding simulation results for the two sets of parameters selected from the script drawing that meet the conditions are as follows:

### Solution1

Performance	Design result	Simulation result
Gain(dB)	24.74	23.05
Gain bandwidth(Hz)	-	501M
$gm_{ID}(S/A)$	5	5.17
$VGS(V)$	0.788	0.788

### Solution2

Performance	Design result	Simulation result
Gain(dB)	22.92	22.91
Gain bandwidth(Hz)	-	469M
$gm_{ID}(S/A)$	5	4.81
$VGS(V)$	0.798	0.818

## Exercise 3

- Design and Script

The purpose of exercise three is mainly to design the maximum gain model. We only need to supplement the corresponding purpose code according to the idea of template code. The detailed code is below:

- 1) Find ft: Use lookup to find ft, and then use a judgment condition to filter the list of ft that meets the condition.
- 2) Obtain av [ i ] = gm / gds: This step is to find out gm and gds respectively through lookup and then directly find the av list that meets the conditions.
- 3) Lookup to find JD: The last step is to find JD through lookup, and iterate W in order to consider the impact of cdd.

```

1 import numpy as np
2 import matplotlib.pyplot as plt
3 from look_up import *
4 nch = importdata ('nch_1v.mat')

5
6 L = nch['L']
7 fu = 5e8
8 CL = 1e-12
9 VDS = 0.55
10 gm_id_range = np.linspace(5, 30, 50)
11 gm_id = []
12 av = []

13
14 for i, l in enumerate(L):
15     # TODO: Find ft
16     ft = look_up_vs_gm_id(nch, 'GM_CGG', gm_id_range, vds=VDS,
17                           l=l) / (2 * np.pi)
18     m = ft >= 10 * fu
19     if np.any(m):
20         gm_id.append(gm_id_range[max(np.where(m == 1)[0])])
21     else:

```



```

21     gm_id.append(float('nan'))
22
23     # TODO: Obtain av[i] = gm / gds
24     gm = look_up_vs_gm_id(nch, 'GM', gm_id[i], vds=VDS, l=l)
25     gds = look_up_vs_gm_id(nch, 'GDS', gm_id[i], vds=VDS, l=l)
26     av.append(gm / gds)
27
28 fig, ax = plt.subplots(1)
29 ax.plot(L, av, label='Av')
30
31 ax.plot(L, gm_id, label='gm/Id')
32 ax.legend()
33 plt.xlabel('Channel Length (L)')
34 plt.title('Gain (Av) and Optimal gm/Id vs. Channel Length (L)')
35 plt.show()
36
37 gm_id_opt = gm_id[np.nanargmax(av)]
38 l_opt = L[np.nanargmax(av)]
39
40 # TODO: Lookup to find JD
41 jd = look_up_vs_gm_id(nch, 'ID_W', gm_id_opt, vds=VDS, l=l_opt)
42
43 cdd_w = look_up_vs_gm_id(nch, 'CDD_W', gm_id_opt, vds=VDS, l=l_opt)
44 cdd = 0
45 for i in range(1, 10):
46     gm_opt = 2 * np.pi * fu * (CL + cdd)
47     ID = gm_opt / gm_id_opt
48     W = ID / jd
49     cdd = W * cdd_w
50
51 print(f"cdd:{cdd}")
52 print(f"gm_opt:{gm_opt}")
53 print(f"gm_id_opt: {gm_id_opt}")
54 print(f"l_opt:{l_opt}")
55
56
57 # Simulation parameter
58 fT_3 = look_up_vs_gm_id(nch, 'GM_CGG', gm_id_opt, vds=VDS,
59                         l=l_opt) / (2 * np.pi)
60 Av_3 = look_up_vs_gm_id(nch, 'GM_GDS', gm_id_opt, vds=VDS, l=l_opt)
61 gds_3 = look_up_vs_gm_id(nch, 'GDS', gm_id_opt, vds=VDS, l=l_opt)
62
63 ro = 1 / gds_3
64 intrinsic_gain_3 = gm_opt * ro
65
66 ID_3 = gm_opt / gm_id_opt
67
68 JD_3 = look_up_vs_gm_id(nch, 'ID_W', gm_id_opt, vds=VDS, l=l_opt)
69 W_3 = ID_3 / JD_3
70 print(f"ID: {ID_3}")
71 VGS_3 = look_up_vgs_vs_gm_id(nch, gm_id_opt, l=l_opt, vds=VDS)
72
73 print(f"Intrinsic Gain: {intrinsic_gain_3}")
74 print(f"fT: {fT_3} Hz")
75 print(f"Width (W): {W_3} m")
76 print(f"Required VGS: {VGS_3} V")

```


- Cadence simulation

Gain4 is for exercise3

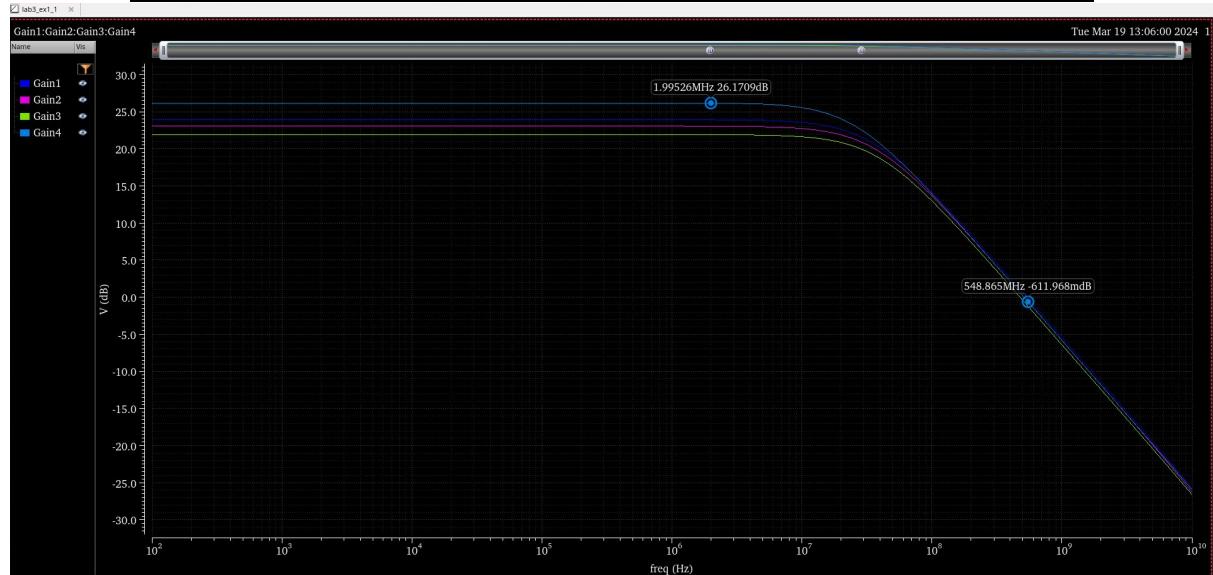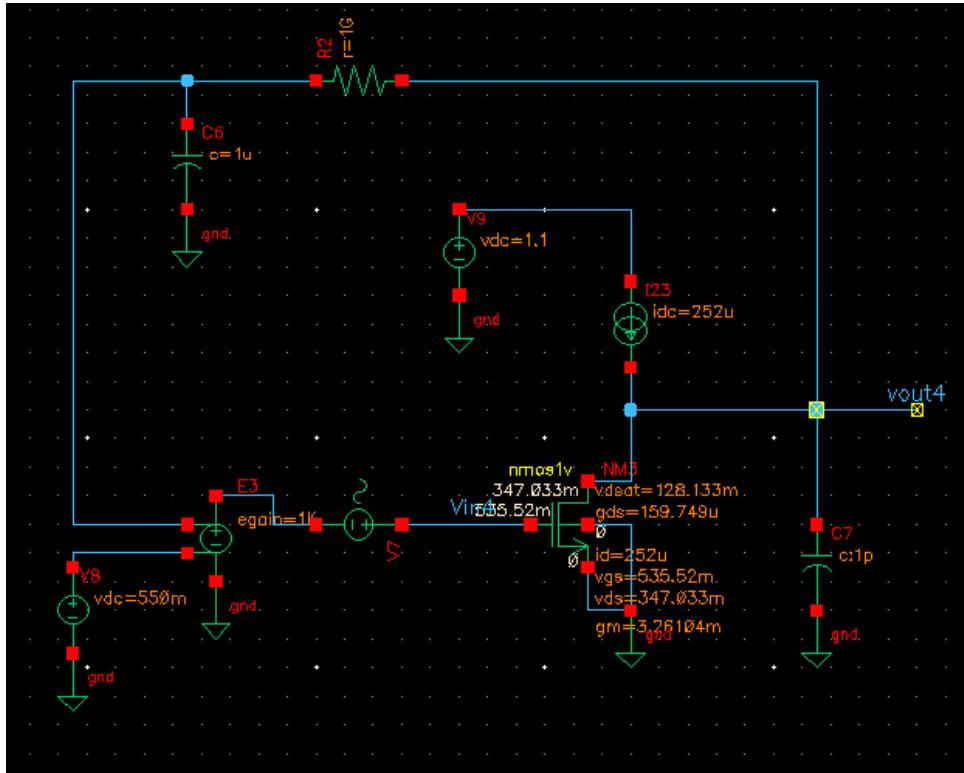

- Analysis of the results

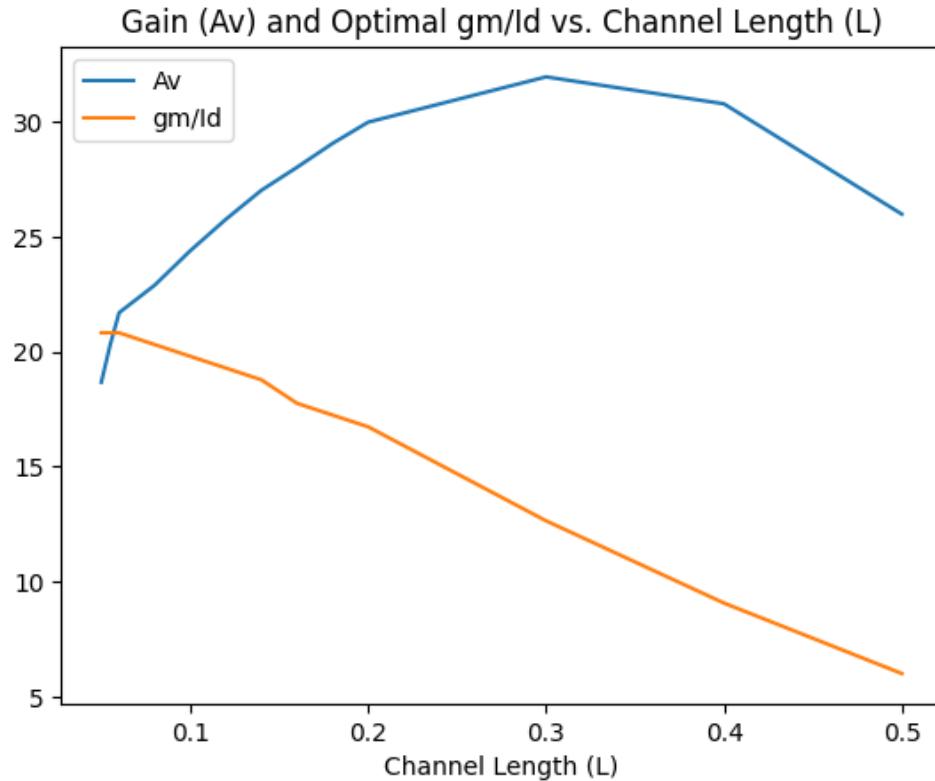The parameters designed in this exercise are simulated, and the simulation result is the Gain4 curve. It can be seen that the Gain4 design is significantly higher than other designs in the 20dB curve. The specific performance results comparison is shown in the table below. It can be found that the gain and cutoff frequency have been improved compared to the previous design.



Performance	Exercise3 Design	Exercise2 Design1	Exercise2 Design2
Gain(dB)	26.17	24.74	22.92
Gain bandwidth(Hz)	548M	501M	470M
$gm_{ID}(S/A)$	12.94	5.17	4.81
$VGS(V)$	0.535	0.818	0.788

## Exercise 4

- Design and Script

For exercise 4, the design of lab1 must be re-simulated first, because the device is replaced with the original part in gpdk045. Regarding the function design part, we need to design according to the conditions of known first, and then encapsulate it into a function.

The specific script implementation is consistent with the idea of exercise3. First, find the  $f_t$  that meets the  $f_u$  condition and its corresponding  $Av$  through the loop of the  $gm_id$  list and the  $L$  list. By selecting the  $L$  corresponding to the maximum  $Av$ , the various parameters of the component are further determined. The specific implementation steps remain the same as the previous exercise.

Script:

```

1 def lab1(fu, CL=1e-12, gm_id_range=np.linspace(5, 30, 50),
2         vds_range=np.linspace(0.35, 1.05, 200)):
3     nch = importdata('nch_1v.mat')
4     L = nch['L']

```

```

4
5     av_matrix = np.zeros((len(gm_id_range), len(L)))
6     vds_opt_matrix = np.zeros((len(gm_id_range), len(L)))
7
8     for i, gm_id in enumerate(gm_id_range):
9         for j, l in enumerate(L):
10            ft = look_up_vs_gm_id(nch, 'GM_CGG', gm_id, l=l) / (2
11                * np.pi)
12            if ft < 10 * fu:
13                av_matrix[i, j] = float('nan')
14                vds_opt_matrix[i, j] = float('nan')
15                continue
16
17            av_values = []
18            for vds in vds_range:
19                gds_id = look_up_vs_gm_id(nch, 'GDS_ID', gm_id,
20                    vds=vds, l=l)
21                av = gm_id / (gds_id + 1/(1.1-vds))
22                av_values.append(av)
23
24            max_av_index = np.argmax(av_values)
25            av_matrix[i, j] = av_values[max_av_index]
26            vds_opt_matrix[i, j] = vds_range[max_av_index]
27
28            max_indices = np.unravel_index(np.nanargmax(av_matrix),
29                av_matrix.shape)
30            max_gm_id_index, max_l_index = max_indices
31            gm_id_opt = gm_id_range[max_gm_id_index]
32            l_opt = L[max_l_index]
33            vds_opt = vds_opt_matrix[max_indices]
34
35            jd = look_up_vs_gm_id(nch, 'ID_W', gm_id_opt, vds=vds_opt,
36                l=l_opt)
37
38            cdd_w = look_up_vs_gm_id(nch, 'CDD_W', gm_id_opt, vds=vds_opt,
39                l=l_opt)
40            cdd = 0
41            for i in range(1, 10):
42                gm_opt = 2 * np.pi * fu * (CL + cdd)
43                ID = gm_opt / gm_id_opt
44                W = ID / jd
45                cdd = W * cdd_w
46
47            result = {
48                'fu': fu,
49                'cdd': cdd,
50                'gm_opt': gm_opt,
51                'gm_id_opt': gm_id_opt,
52                'l_opt': l_opt,
53                'vds_opt': vds_opt,
54                'ID': ID,
55                'VGS': look_up_vgs_vs_gm_id(nch, gm_id_opt, l=l_opt,
56                    vds=vds_opt),
57                'RD': (1.1 - vds_opt) / ID,
58                'W': W
59            }

```

```
55     return result
```

The following is a test of the lab1 function script based on the fu list given in the question, and the return value is obtained.

```
1 fu_list = [1e6, 50e6, 100e6, 500e6, 1e9]
2 results = [lab1(fu) for fu in fu_list]
3
4 for result in results:
5     print(f"fu: {result['fu']/1e6} MHz")
6     print(f"cdd: {result['cdd']}")  

7     print(f"gm_opt: {result['gm_opt']}")  

8     print(f"gm_id_opt: {result['gm_id_opt']}")  

9     print(f"l_opt: {result['l_opt']}")  

10    print(f"vds_opt: {result['vds_opt']}")  

11    print(f"ID: {result['ID']}")  


12    print(f"VGS: {result['VGS']}")  



13    print(f"RD: {result['RD']}")  

14    print(f"W:{result['W']}")
```
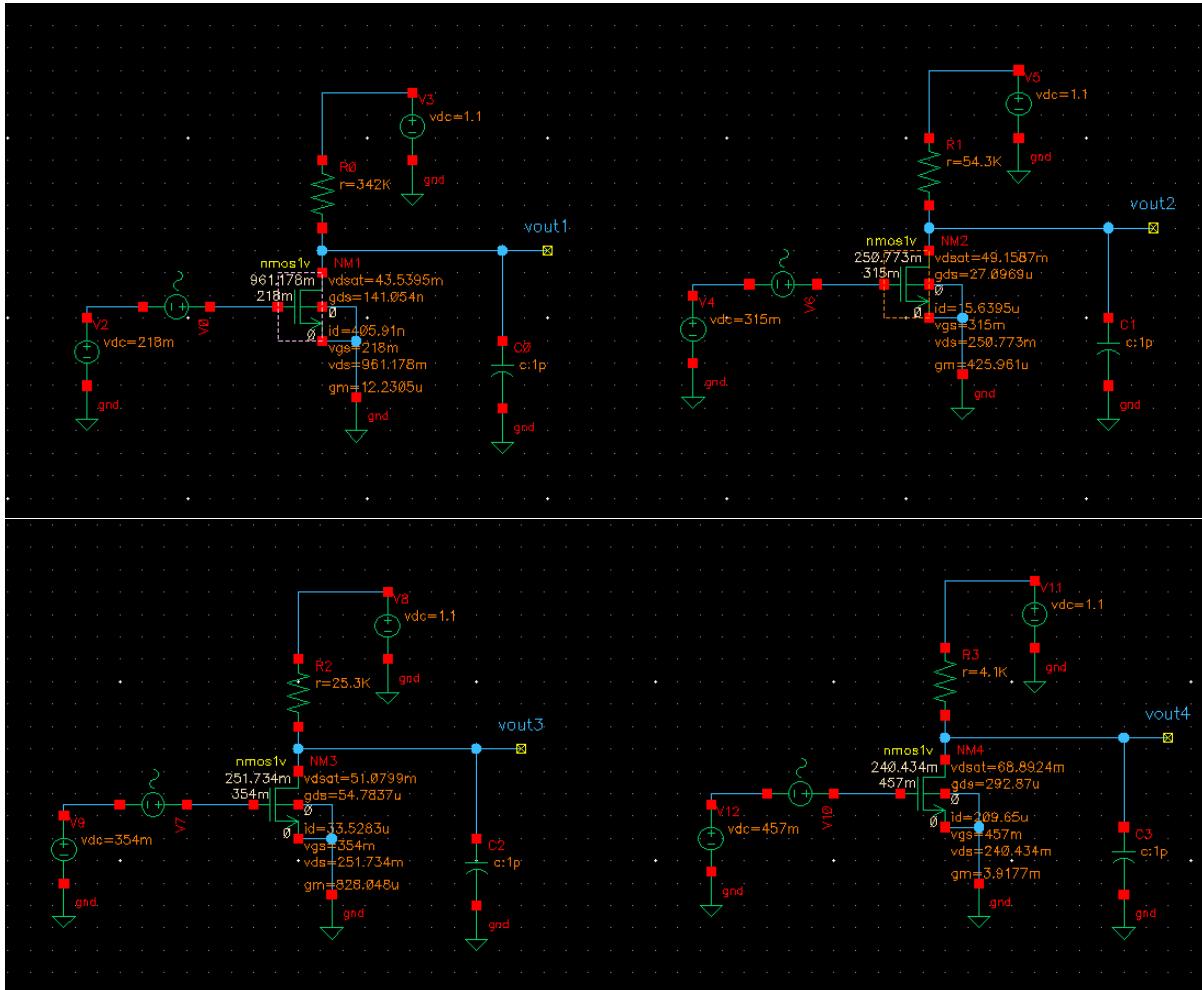
### • Cadence simulation

Gain1-Gain5 are the five frequencies required by the question. We use the parameters obtained from the script to simulate the circuit diagram.



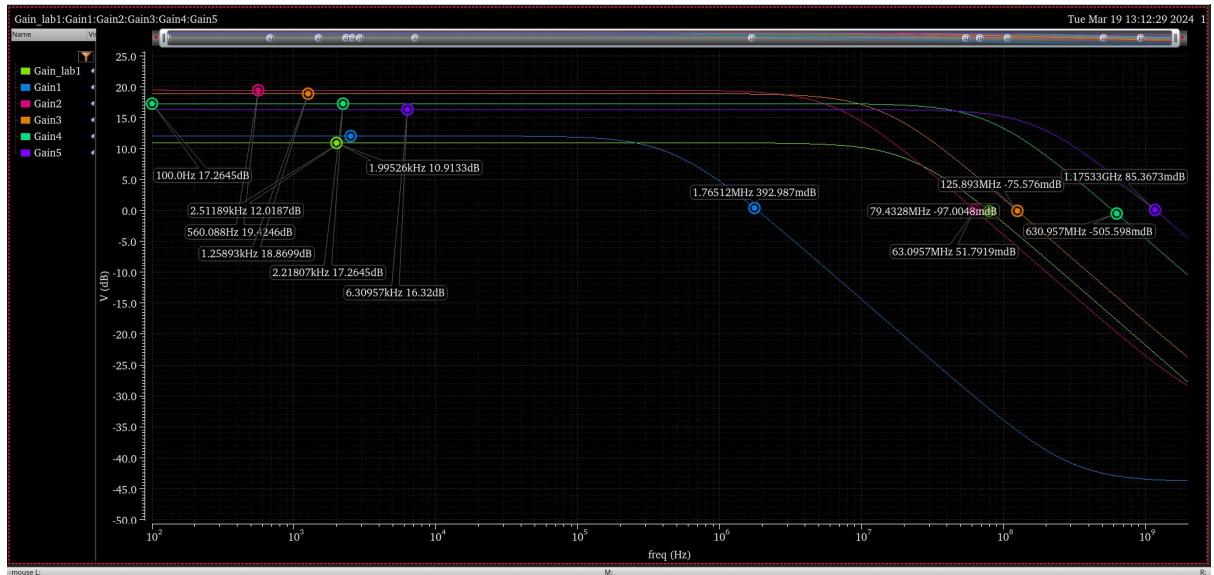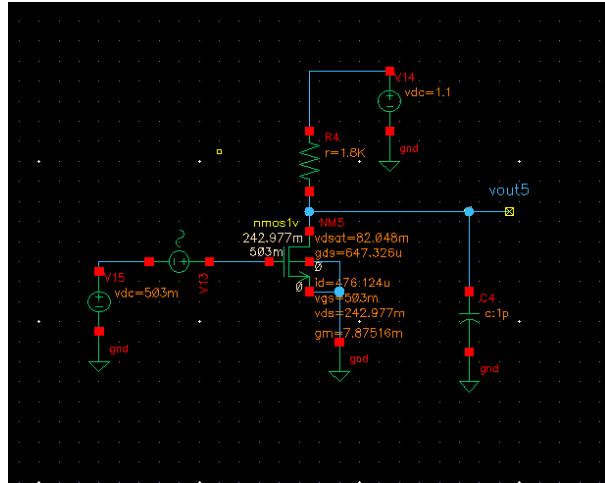

## • Analysis of the results

The simulation results obtained according to the requirements are drawn into a table, and the performance of each result is displayed as follows:

Parameter	1 MHz	50 MHz	100 MHz	500 MHz	1 GHz
VGS(V)	218m	315m	354m	457m	503m
RD( $\Omega$ )	342k	54.3k	25.3k	4.1k	1.8k
W( $\mu m$ )	27.66	144.55	115.82	83.71	86.38
L( $\mu nm$ )	1.0	0.14	0.14	0.14	0.12
I(A)	405.91n	15.64u	33.53u	209.65u	472.16u
gm/ID(S/A)	30.19	27.24	24.69	18.69	16.54
Gain (dB)	12.02	19.42	18.87	17.26	16.32
Gain bandwidth (Hz)	1.77M	63.10M	125.89M	630.96M	1.17G

## Exercise 5

- Design and Script

For the redesign of lab2, we first use the same logic script code to find the corresponding optimal parameters as before.

My draft derivation is as follows. As mentioned in the lab, first the expression of  $A_v$  is given, which is related to the three controllable parameters of  $g_{mid}$ ,  $g_{dsid}$  and  $v_{out}$ , where  $v_{out}$  is the vds of nmos. So we can control the range of  $v_{out}$ , construct an outermost loop for  $v_{out}$  to find the maximum  $A_v$ . Inside this loop, we still use the logic from our previous exercise to draw the relationship between  $A_v$  and  $L$  for  $g_{mid}$  and  $g_{dsid}$ . After finding this  $L$ , find the corresponding parameters through lookup. Another thing to note is that PMOS and NMOS appear at the same time in this exercise, so the search for their parameters needs to be done separately. Here, first set up the PMOS cycle, then find the PMOS parameters and  $v_{gs}$  that maximize the gain, and then find the NMOS parameters.

$$f_T = \frac{g_m}{C_{gg}}, \quad C_{gg} = C_{gs} + C_{gd} + C_{gb} \quad \text{frequency range} \leq \frac{f_T}{10}$$

$$\begin{aligned} f_T: 1.5 \times 10^{10} \text{ Hz} & \quad f_M = 500 \text{ MHz} \\ \underbrace{\text{maximum}}_{f_M \leq f_T/10} & \quad = 5 \times 10^2 \times 10^6 \text{ Hz} \\ f_T \geq 10 f_M & \quad = 5 \times 10^9 \text{ Hz} \end{aligned}$$

$$\begin{aligned} A &= \frac{g_m / I_D}{g_{ds} + \frac{I_D}{V_{DD} - V_{out}}} \\ &= \frac{g_m / I_D}{(g_{ds} / I_D) + \frac{1}{V_{DD} - V_{out}}} \end{aligned}$$

$$\begin{aligned} A &= g_{mn} \left\{ \frac{1}{R_s} + \frac{1}{R_L} \right\}^{-1} \\ &= \left( g_{ds} + \frac{I_o}{V_{DD} - V_{out}} \right)^{-1} \\ &= g_{mn} \left( \frac{1}{g_{ds}} + \frac{I_o}{V_{DD} - V_{out}} \right) \end{aligned}$$

①  $g_{m-ID}$ .  $\xrightarrow{\text{loop 1}}$   $\xrightarrow{\text{loop 2}}$   $\xrightarrow{\text{loop 3}}$

②  $g_{ds-ID}$ .

③ sweep  $V_{out}$ .

for  $l$  in  $L$ . loop 1

for  $i$  in  $g_{m-ID}$ -range. loop 2.

$g_{ds-ID}$ .

$A_v = \frac{g_{m-ID}(i,j)}{g_{ds-ID}(i,j) + \frac{1}{L_i - V_{out}}} \xrightarrow{\text{loop 3.}}$

For gain  $A_v$ :

$$\begin{aligned} g_{mn} &= (\mu_n C_{ox}) n \left( \frac{W}{L} \right)_n V_{out} \\ &= (\mu_n C_{ox}) n \left( \frac{W}{L} \right)_n (V_{gs} - V_T) \end{aligned}$$

$$\begin{aligned} r_{on} &= \frac{1}{\lambda_n I_o}, \quad r_{op} = \frac{1}{\lambda_p I_o} \\ \therefore r_{on}/r_{op} &= \frac{\frac{1}{\lambda_n I_o} \cdot \frac{1}{\lambda_p I_o}}{\frac{1}{\lambda_n I_o} + \frac{1}{\lambda_p I_o}} = \frac{\frac{1}{\lambda_n \lambda_p I_o^2}}{\frac{\lambda_n + \lambda_p}{\lambda_n \lambda_p I_o}} = \frac{1}{(\lambda_n + \lambda_p) I_o} \end{aligned}$$

$$\therefore A_v = \frac{g_{mn}}{(\lambda_n + \lambda_p) I_o} = \frac{\mu_n C_{ox} \frac{W}{L} V_{out}}{(\lambda_n + \lambda_p) \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{out}^2} = \frac{2}{V_{out} (\lambda_n + \lambda_p)}$$

Script

```

1 import numpy as np
2 import matplotlib.pyplot as plt
3 from look_up import *

```

```

4
5 fu = 1e9
6 CL = 1e-12
7 VDD = 1.1
8 Vout_range = np.linspace(0.1, 1.0, 100)
9
10 pch = importdata('pch_1v.mat')
11 nch = importdata('nch_1v.mat')
12 Lp = pch['L']
13 Ln = nch['L']
14
15 best_av_max = -np.inf
16 best_results = None
17
18 for Vout in Vout_range:
19     VGS_p = VDS_p = VDD - Vout
20
21     best_av_p = -np.inf
22     best_pmos = None
23
24     for l_p in Lp:
25         gm_id_range = np.linspace(5, 30, 50)
26         ft_p = look_up_vs_gm_id(pch, 'GM_CGG', gm_id_range,
27             vds=VDS_p, l=l_p) / (2 * np.pi)
28         m = ft_p >= fu
29
30         if np.any(m):
31             gm_id_p = gm_id_range[np.max(np.where(m))]
32             gds_id_p = look_up_vs_gm_id(pch, 'GDS_ID', gm_id_p,
33                 vds=VDS_p, l=l_p)
34
35             best_av_n = -np.inf
36             best_nmos = None
37
38             for l_n in Ln:
39                 gm_id_range = np.linspace(5, 30, 50)
40                 ft_n = look_up_vs_gm_id(nch, 'GM_CGG',
41                     gm_id_range, vds=Vout, l=l_n) / (2 * np.pi)
42                 m = ft_n >= fu
43
44                 if np.any(m):
45                     gm_id_n = gm_id_range[np.max(np.where(m))]
46                     gds_id_n = look_up_vs_gm_id(nch, 'GDS_ID',
47                         gm_id_n, vds=Vout, l=l_n)
48                     gm_n = look_up_vs_gm_id(nch, 'GM', gm_id_n,
49                         vds=Vout, l=l_n)
50                     RL = 1 / ((VDD - Vout) / (gm_id_n / gm_n))
51                     av = gm_id_n / (gds_id_n + gds_id_p + 1/RL)
52
53                     if av > best_av_n:
54                         best_av_n = av
55                         best_nmos = {
56                             'gm_id_n': gm_id_n,
57                             'l_n': l_n
58                         }

```



```

55         if best_nmos is not None and best_av_n > best_av_p:
56             best_av_p = best_av_n
57             best_pmos = {
58                 'gm_id_p': gm_id_p,
59                 'l_p': l_p
60             }
61
62     if best_pmos is not None and best_av_p > best_av_max:
63         best_av_max = best_av_p
64         best_results = {
65             'fu',
66             'gm_id_opt_p': best_pmos['gm_id_p'],
67             'gm_id_opt_n': best_nmos['gm_id_n'],
68             'l_opt_p': best_pmos['l_p'],
69             'l_opt_n': best_nmos['l_n'],
70             'vout_opt': Vout,
71             'VGS_p': VGS_p,
72             'VDS_p': VDS_p,
73             'av_max': best_av_p
74         }
75
76     if best_results is not None:
77         gm_id_opt_p = best_results['gm_id_opt_p']
78         gm_id_opt_n = best_results['gm_id_opt_n']
79         l_opt_p = best_results['l_opt_p']
80         l_opt_n = best_results['l_opt_n']
81         vout_opt = best_results['vout_opt']
82         VGS_p = best_results['VGS_p']
83         VDS_p = best_results['VDS_p']
84         VGS_n = vout_opt
85
86         jd_n = look_up_vs_gm_id(nch, 'ID_W', gm_id_opt_n,
87             vds=vout_opt, l=l_opt_n)
88         jd_p = look_up_vs_gm_id(pch, 'ID_W', gm_id_opt_p, vds=VDS_p,
89             l=l_opt_p)
90
91         cdd_w_n = look_up_vs_gm_id(nch, 'CDD_W', gm_id_opt_n,
92             vds=vout_opt, l=l_opt_n)
93         cdd_w_p = look_up_vs_gm_id(pch, 'CDD_W', gm_id_opt_p,
94             vds=VDS_p, l=l_opt_p)
95
96         cdd_n = cdd_p = 0
97         for i in range(1, 10):
98             gm_opt_n = 2 * np.pi * fu * (CL/2 + cdd_n)
99             gm_opt_p = 2 * np.pi * fu * (CL/2 + cdd_p)
100            ID = gm_opt_n / gm_id_opt_n
101            W_n = ID / jd_n
102            W_p = ID / jd_p
103            cdd_n = W_n * cdd_w_n
104            cdd_p = W_p * cdd_w_p
105
106    best_results['cdd_n'] = cdd_n
107    best_results['cdd_p'] = cdd_p
108    best_results['gm_n'] = gm_opt_n
109    best_results['gm_p'] = gm_opt_p
110    best_results['VGS_n'] = VGS_n

```

```
107     best_results['ID'] = ID
108     best_results['W_n'] = W_n
109     best_results['W_p'] = W_p
110
111     for key, value in best_results.items():
112         print(f"{key}: {value}")
113 else:
114     print("No valid results found.")
```

- Cadence simulation

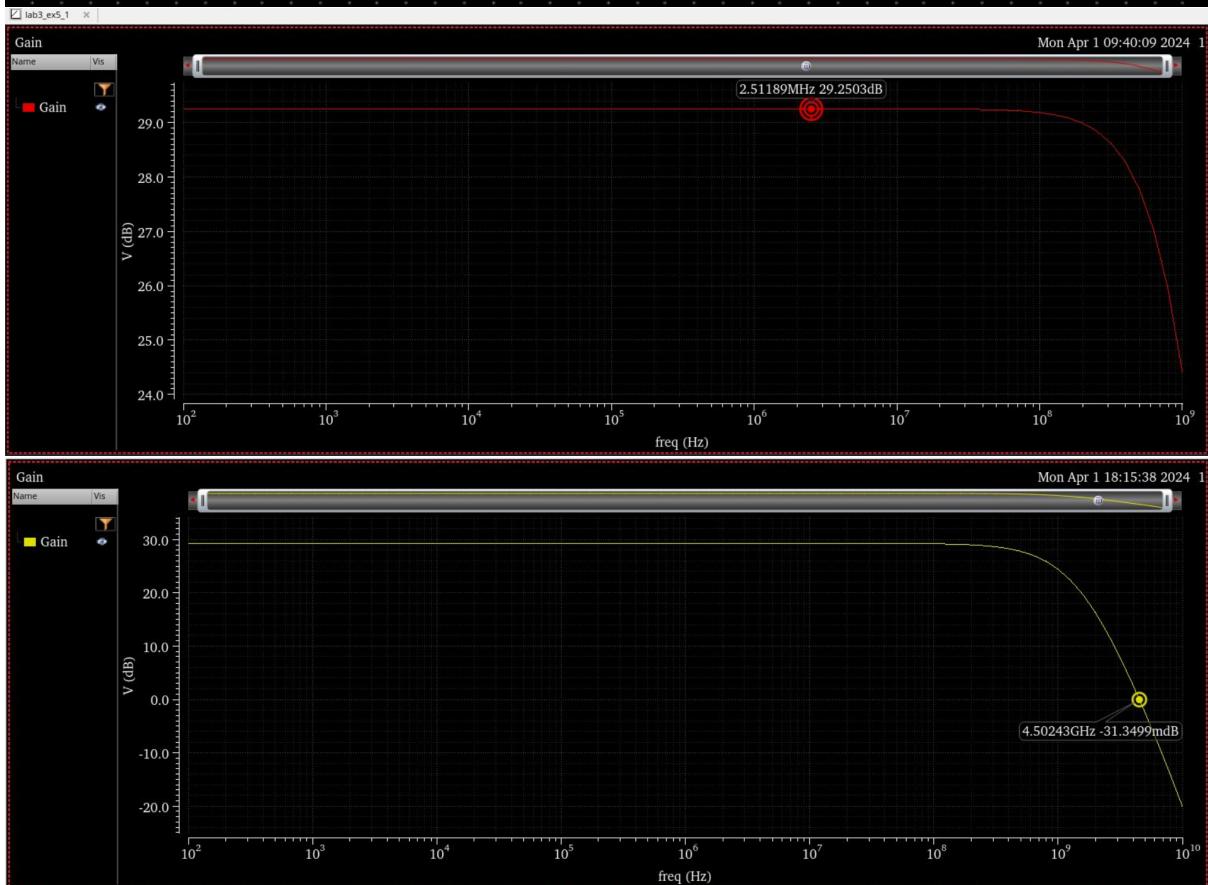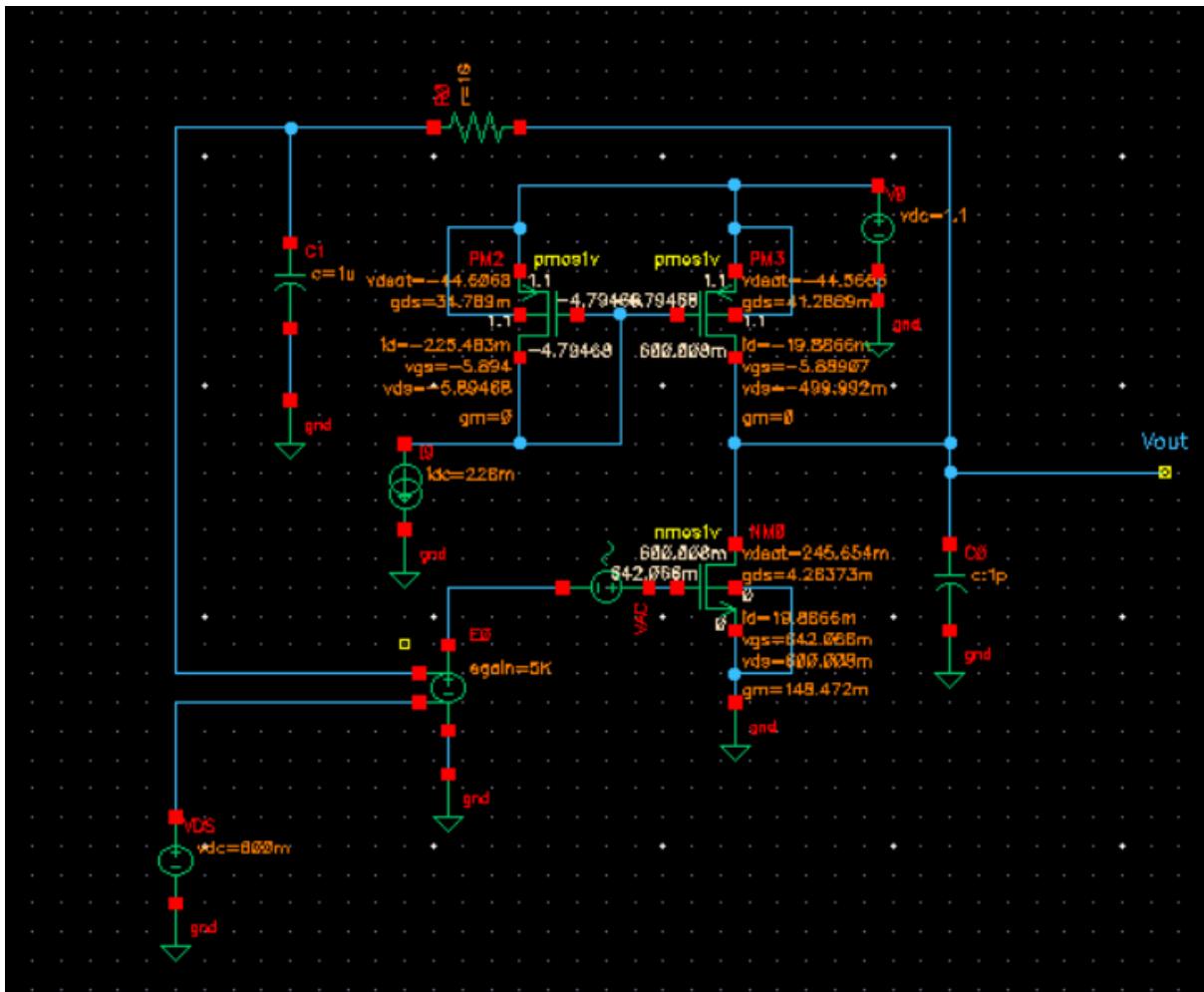

- **Analysis of the results**

For hand calculation, the gain can be calculated directly using this formula:  $A_v = g_m n (r_{on} // r_{op})$ .

In lab2, the results obtained by manual calculation and experiment are not much different, but in exercise 4, the simulation results obtained are obviously very different from lab2. This is because the devices used are different and the parameters set are completely different.

Performance	Handout result in lab2	Simulation result for ex4
Gain(dB)	44.372	29.25
Gain bandwidth(Hz)	1.95M	4.5G

## Exercise 6

- **Design and Script**

For ex6 design and script improvement:

- For NMOS, we use  $V_{GS\_n} = V_{ICM}$  as the gate voltage since the source is now connected to the tail current source.
- When calculating  $R_L$ , we use  $R_L = \frac{1}{(V_{DD} - V_{out})/(2*g_m * id_n / g_m)} = \frac{1}{(V_{DD} - V_{out})/(2*g_m * id_n / g_m)}$  because in differential mode, the load resistance is twice the single-ended value.
- When calculating the gain  $a_v$ , we use  $a_v = \frac{g_m * id_n}{2*(gds\_id\_n + gds\_id\_p) + 1/R_L}$ , because in differential mode, the transconductance is twice the single-ended value, and the output conductance is the single-ended value doubled.
- In the `best_results` dictionary, I added '`VICM_opt`': `VICM` and '`VGS_n`': `VGS_n` key-value pairs to store the best input common mode voltage and gate voltage of the NMOS.

Script:

```

1 import numpy as np
2 import matplotlib.pyplot as plt
3 from look_up import *
4
5 fu = 1e9
6 CL = 1e-12
7 VDD = 1.1
8 Vout_range = np.linspace(0.1, 1.0, 100)
9 VICM = 0.6 #Set a suitable input common mode voltage
10
11 pch = importdata('pch_1v.mat')
12 nch = importdata('nch_1v.mat')
13 Lp = pch['L']
14 Ln = nch['L']
15
16 # Step 1: Search for the optimal parameters of the differential
17 # amplifier circuit
17 best_av_max = -np.inf
18 best_results = None
19
20 for Vout in Vout_range:
21     VGS_p = VDS_p = VDD - Vout
22     VGS_n = VICM
23

```

```

24     best_av_p = -np.inf
25     best_pmos = None
26
27     for l_p in Lp:
28         gm_id_range = np.linspace(5, 30, 50)
29         ft_p = look_up_vs_gm_id(pch, 'GM_CGG', gm_id_range,
30             vds=VDS_p, l=l_p) / (2 * np.pi)
31         m = ft_p >= fu
32
33         if np.any(m):
34             gm_id_p = gm_id_range[np.max(np.where(m))]
35             gds_id_p = look_up_vs_gm_id(pch, 'GDS_ID', gm_id_p,
36                 vds=VDS_p, l=l_p)
37
38             best_av_n = -np.inf
39             best_nmos = None
40
41             for l_n in Ln:
42                 gm_id_range = np.linspace(5, 30, 50)
43                 ft_n = look_up_vs_gm_id(nch, 'GM_CGG',
44                     gm_id_range, vds=VGS_n, l=l_n) / (2 * np.pi)
45                 m = ft_n >= fu
46
47                 if np.any(m):
48                     gm_id_n = gm_id_range[np.max(np.where(m))]
49                     gds_id_n = look_up_vs_gm_id(nch, 'GDS_ID',
50                         gm_id_n, vds=VGS_n, l=l_n)
51                     gm_n = look_up_vs_gm_id(nch, 'GM', gm_id_n,
52                         vds=VGS_n, l=l_n)
53                     RL = 1 / ((VDD - Vout) / (2 * gm_id_n / gm_n))
54                     av = gm_id_n / (2 * (gds_id_n + gds_id_p) +
55                         1/RL)
56
57                     if av > best_av_n:
58                         best_av_n = av
59                         best_nmos = {
60                             'gm_id_n': gm_id_n,
61                             'l_n': l_n
62                         }
63
64
65             if best_nmos is not None and best_av_n > best_av_p:
66                 best_av_p = best_av_n
67                 best_pmos = {
68                     'gm_id_p': gm_id_p,
69                     'l_p': l_p
70                 }
71
72
73     if best_pmos is not None and best_av_p > best_av_max:
74         best_av_max = best_av_p
75         best_results = {
76             'fu': fu,
77             'gm_id_opt_p': best_pmos['gm_id_p'],
78             'gm_id_opt_n': best_nmos['gm_id_n'],
79             'l_opt_p': best_pmos['l_p'],
80             'l_opt_n': best_nmos['l_n'],
81             'vout_opt': Vout,

```

```

74         'VGS_p': VGS_p,
75         'VDS_p': VDS_p,
76         'VGS_n': VGS_n,
77         'av_max': best_av_p
78     }
79
80 # Step 2: Use the optimal parameters of the differential amplifier
81 # circuit to search for the optimal parameters of the current
82 # mirror
83 if best_results is not None:
84     gm_id_opt_p = best_results['gm_id_opt_p']
85     gm_id_opt_n = best_results['gm_id_opt_n']
86     l_opt_p = best_results['l_opt_p']
87     l_opt_n = best_results['l_opt_n']
88     vout_opt = best_results['vout_opt']
89     VGS_p = best_results['VGS_p']
90     VDS_p = best_results['VDS_p']
91     VGS_n = best_results['VGS_n']
92
93     jd_n = look_up_vs_gm_id(nch, 'ID_W', gm_id_opt_n, vds=VGS_n,
94                             l=l_opt_n)
95     jd_p = look_up_vs_gm_id(pch, 'ID_W', gm_id_opt_p, vds=VDS_p,
96                             l=l_opt_p)
97
98     cdd_w_n = look_up_vs_gm_id(nch, 'CDD_W', gm_id_opt_n,
99                                 vds=VGS_n, l=l_opt_n)
100    cdd_w_p = look_up_vs_gm_id(pch, 'CDD_W', gm_id_opt_p,
101                                vds=VDS_p, l=l_opt_p)
102
103    best_IM_max = -np.inf
104    best_IM_results = None
105
106    for l_IM in Lp:
107        gm_id_range = np.linspace(5, 30, 50)
108        ft_IM = look_up_vs_gm_id(pch, 'GM_CGG', gm_id_range,
109                                vds=VDS_p, l=l_IM) / (2 * np.pi)
110        m = ft_IM >= fu
111
112        if np.any(m):
113            gm_id_IM = gm_id_range[np.max(np.where(m))]
114            gds_id_IM = look_up_vs_gm_id(pch, 'GDS_ID', gm_id_IM,
115                                         vds=VDS_p, l=l_IM)
116            IM_av = gm_id_IM / gds_id_IM
117
118            if IM_av > best_IM_max:
119                best_IM_max = IM_av
120                best_IM_results = {
121                    'gm_id_IM': gm_id_IM,
122                    'l_IM': l_IM,
123                    'IM_av': IM_av
124                }
125
126    if best_IM_results is not None:
127        gm_id_IM = best_IM_results['gm_id_IM']
128        l_IM = best_IM_results['l_IM']
129        IM_av = best_IM_results['IM_av']


```

```

122
123     jd_IM = look_up_vs_gm_id(pch, 'ID_W', gm_id_IM, vds=VDS_p,
124                               l=l_IM)
125     cdd_w_IM = look_up_vs_gm_id(pch, 'CDD_W', gm_id_IM,
126                                   vds=VDS_p, l=l_IM)
127
128     cdd_n = cdd_p = cdd_IM = 0
129     for i in range(1, 10):
130         gm_opt_n = 2 * np.pi * fu * (CL/2 + cdd_n)
131         gm_opt_p = 2 * np.pi * fu * (CL/2 + cdd_p)
132         ID = gm_opt_n / gm_id_opt_n
133         W_n = ID / jd_n
134         W_p = ID / jd_p
135         W_IM = ID / jd_IM
136         cdd_n = W_n * cdd_w_n
137         cdd_p = W_p * cdd_w_p
138         cdd_IM = W_IM * cdd_w_IM
139
140         best_results['cdd_n'] = cdd_n
141         best_results['cdd_p'] = cdd_p
142         best_results['cdd_IM'] = cdd_IM
143         best_results['gm_n'] = gm_opt_n
144         best_results['gm_p'] = gm_opt_p
145         best_results['ID'] = ID
146         best_results['W_n'] = W_n
147         best_results['W_p'] = W_p
148         best_results['W_IM'] = W_IM
149         best_results['gm_id_IM'] = gm_id_IM
150         best_results['l_IM'] = l_IM
151         best_results['IM_av'] = IM_av
152
153     for key, value in best_results.items():
154         print(f"{key}: {value}")
155     else:
156         print("No valid results found for current mirror.")
157 else:
158     print("No valid results found for differential amplifier.")

```

- Cadence simulation

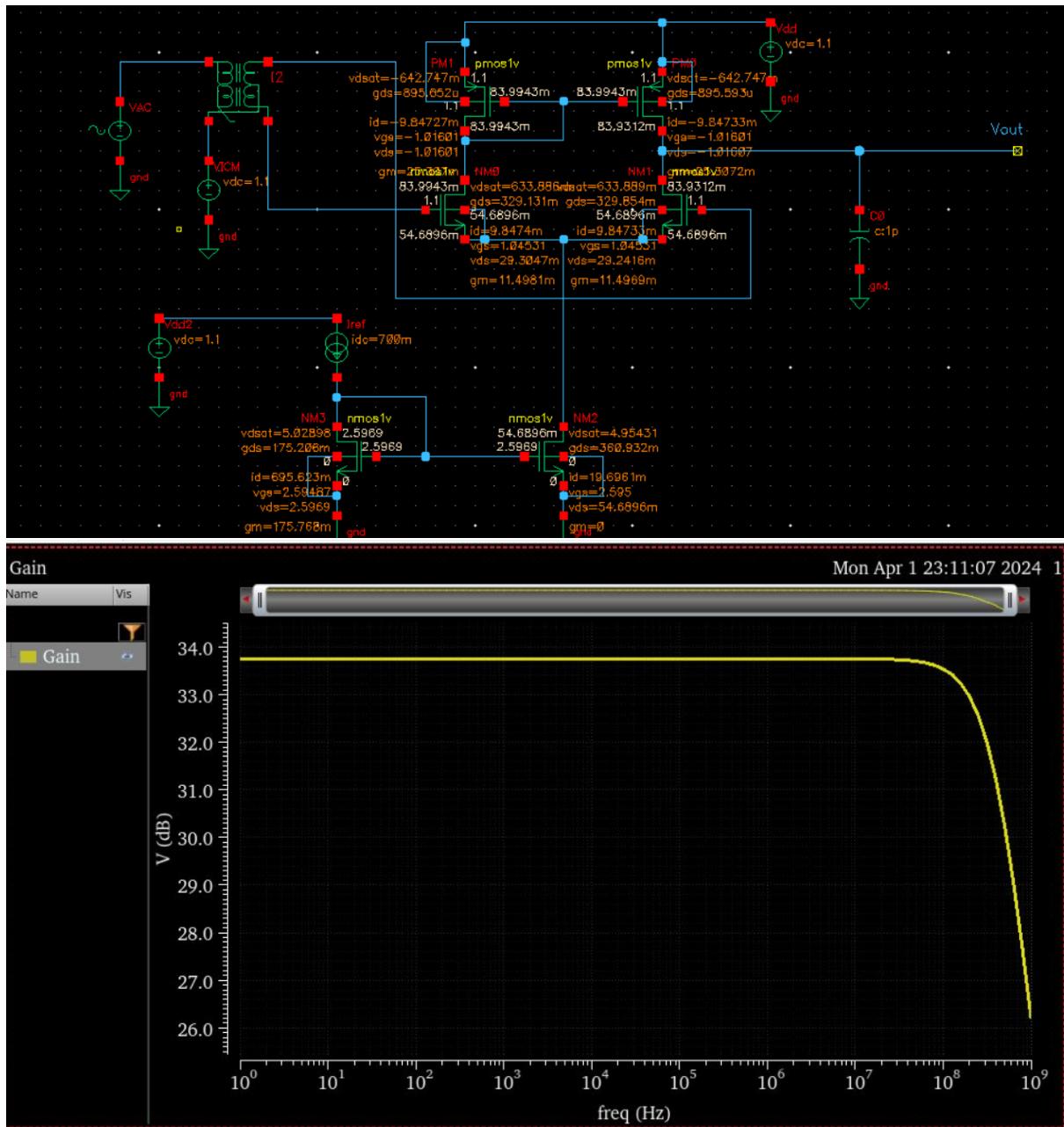

- Analysis of the results

This is a simple design, and better implementation will be improved in the project. Due to the time limit of the experimental report, the simulation has not been perfectly realized, that is, it has not yet reached the computational requirements.